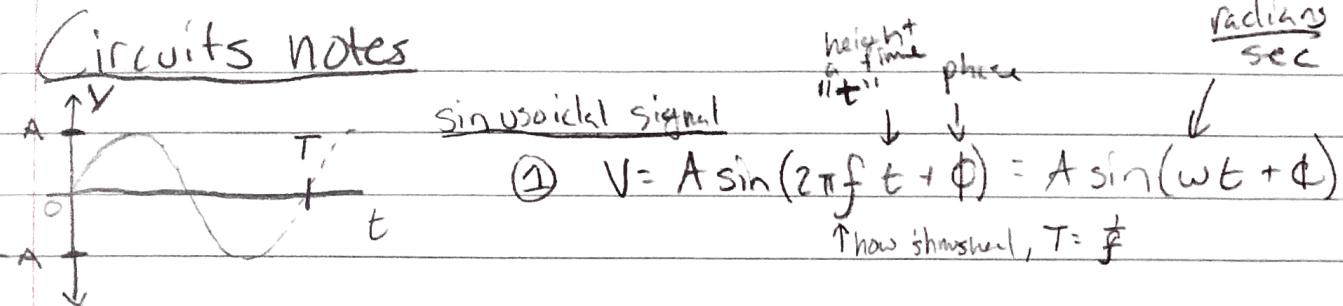


AC, capacitance review

Circuits notes



Ways to specify amplitude $\rightarrow A$, peak to peak $\rightarrow A_{pp} = 2A$, Arms $= \frac{A}{\sqrt{2}}$

(Ex) \rightarrow power dissipated in a resistor given the sinusoidal varying voltage,

\hookrightarrow can't use $P = IV = \frac{V^2}{R} = I^2 R$ since voltage is changing constantly.

\hookrightarrow (instead calculate) $P = \frac{1}{T} \int_0^T \frac{V^2}{R} dt =$ plug in $V = A \sin(\omega t)$ and compute $= \frac{A^2}{2R} = \frac{A_{rms}^2}{R}$

*remember A corresponds to peak voltage so we can use $P = \frac{V^2}{R}$

IF we only use Arms.

Capacitor Review * a capacitor is 2 conducting plates $\left(\frac{\text{Coulombs}}{\text{Volt}} \right)$

- for parallel plates $C = \epsilon \frac{A}{d}$, A is area, d is distance, ϵ is dielectric constant

- a capacitor is a charge storage device


- when a voltage V is applied, a charge Q is stored

$$\hookrightarrow Q = CV$$

- In electronics we care] $\rightarrow I = \frac{dQ}{dt}$, $\frac{dQ}{dt} = C \frac{dV}{dt} = I$
(usually concerned w/ currents)

Series $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$

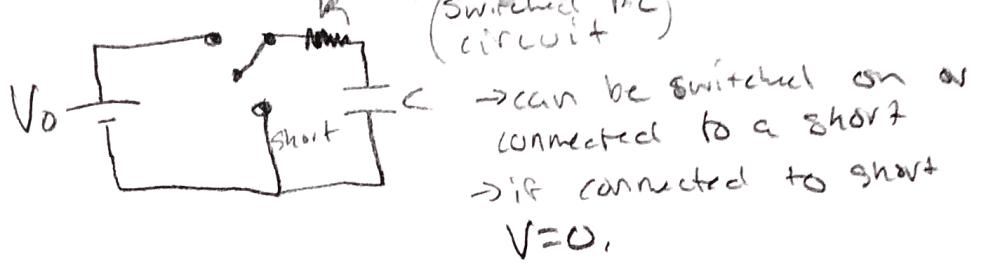Parallel $C_{eq} = C_1 + C_2 + C_3 + \dots + C_n$



RC circuits Review

$$\text{KVL} \quad V = IR + \frac{Q}{C}, \quad (V = V_0 \text{ or } 0)$$

$$(\text{take time derivative}) \quad 0 = R \frac{dI}{dt} + \frac{I}{C} \quad \leftarrow \begin{array}{l} \text{same for} \\ \text{either case} \end{array} \Rightarrow \boxed{\frac{dI}{I} = -\frac{dt}{RC}}$$

Integration: $\ln(I) = -\frac{t}{RC} + K$ constant of integration

$$\downarrow \quad \left(-\frac{t}{RC} + K \right)$$

$$I = e^{K - \frac{t}{RC}} = e^K e^{-\frac{t}{RC}} = I_0 e^{-\frac{t}{RC}}$$

plugging in

Voltage across resistor is just IR → Voltage across capacitor? $\rightarrow V_C = ?$

KVL: $V_C = V - IR$ (either V_0 or 0)

eq 1 → $V_C = V - I_0 R e^{-\frac{t}{RC}}$

or general form after $-t$: $V_C = V_0 e^{-\frac{t}{RC}} + V_2$

Charging $\rightarrow V_C$ is 0 at $t=0$ and $V=V_0$

from eq 1: $0 = V_0 - I_0 R \rightarrow I_0 = \frac{V_0}{R}$

then

$$I = \frac{V_0}{R} e^{-\frac{t}{RC}} \quad \text{and} \quad V_C = V_0 \left[1 - e^{-\frac{t}{RC}} \right]$$

discharging \rightarrow now connect short at $t=0$, $V_C = V_0$ and $V=0$

$$V_0 = 0 - I_0 R \rightarrow I_0 = -\frac{V_0}{R} \quad \text{so}$$

$$I = -\frac{V_0}{R} e^{-\frac{t}{RC}} \quad \text{and} \quad V_C = V_0 e^{-\frac{t}{RC}}$$

current is reversed

voltage is decreasing

ALTERNATING Current

$$(V_{in} = V_p \sin(\omega t)) \quad (V_{in} = V_p \cos(\omega t))$$

*Whether or not we imaginary or for get some answer but look different *

You can have a sin drive or a cos drive, both give you different final solutions. They will have the same magnitude though, $V(t) = \sin(\omega t)$ for all

Pure Resistive load

$$\text{V}_{RL} = \frac{V_R(t)}{V_{in}(\omega t)}$$

$$V(t) - V_R(t) = 0, V(t) = I_R(t)R = V_R(t)$$

$$\text{also: } I(t) = \frac{V_R(t)}{R} = \frac{V_{in}}{R} \sin(\omega t) = I_{in} \sin(\omega t)$$

$$I, V \text{ in phase} \rightarrow \boxed{q=0}$$

$$I_{in} = \frac{V_{in}}{R}, \text{ doesn't depend on } \omega \rightarrow \boxed{X_R = 0}$$

Pure Capacitive load

$$\text{KVL: } V(t) - V_C(t) = 0 \rightarrow V(t) = \frac{Q(t)}{C}$$

$$Q(t) = CV(t) = C V_C(t) = C V_0 \sin(\omega t)$$

$$\frac{dQ(t)}{dt} = I_C(t) = \omega C V_0 \cos(\omega t) \quad \begin{matrix} \text{convert to} \\ \text{sin} \end{matrix}$$

$$I_C(t) = \omega C V_0 \sin(\omega t + \frac{\pi}{2})$$

$$\rightarrow I_{in} = \omega C V_0 \rightarrow X_C = \frac{1}{\omega C} \quad \phi = -\frac{\pi}{2}$$

$$V_{in} = I_{in} X_C$$

Pure Inductive load

$$\text{KVL: } V(t) - V_L(t) = 0, V(t) = L \frac{dI}{dt} = 0$$

$$I_L(t) = \int \frac{V_0}{L} \sin(\omega t) dt = I_L(t) = \frac{V_0}{WL} \cos(\omega t)$$

$$\text{Using } -\cos(\theta) = \sin(\theta - \frac{\pi}{2}) \text{ like before}$$

$$I_L(t) = \frac{V_0}{WL} \sin(\omega t - \frac{\pi}{2}), \phi = +\frac{\pi}{2}$$

$$\rightarrow I_{in} = \frac{V_0}{WL} \rightarrow X_L = WL$$

X_x = Reactance its the real value and its as if the GLR was a resistor by Ohms law
Imaginary part of impedance, for AC current only, (how much device fights AC) (resistor doesn't)

Impedance, $V(t) = V_p \cos(\omega t) \rightarrow \hat{V}(t) = V_p e^{j\omega t}$

$$\hat{Z} = \frac{\hat{V}(t)}{\hat{I}(t)} = \frac{V_p}{I_p} e^{-j\theta} \quad \begin{matrix} \text{this writing to be} \\ \text{taken in the ().} \end{matrix}$$

$$\text{Re}(\hat{e}^{j\theta}) = \cos\theta + j\sin\theta \quad \text{proj onto Real axis}$$

* can take $\text{Re}(\hat{e}^{j\theta})$ before or after derivative

$d \text{Re}(\hat{e}^{j\theta}) / d\theta = \text{Re}(\hat{e}^{j\theta})$ prove by subbing, $e^{j\theta} = \cos\theta + j\sin\theta$

$\text{CSA} = -\sin\theta$, $Z_m = R$ (no mag part)

Capacitor Impedance

$$q(t) = CV(t) \rightarrow \frac{dq}{dt} = C \frac{dV(t)}{dt}$$

$$\hat{q}(t) = C \frac{dV(t)}{dt} \leftarrow \hat{V}(t) = V_p e^{j\omega t}$$

$$\hat{q}(t) = C V_p j\omega e^{j\omega t} = C j\omega \hat{V}(t)$$

$$\hat{Z}_C = \frac{\hat{V}(t)}{\hat{q}(t)} = \frac{1}{j\omega C}$$

Inductor Impedance

$$V(t) = L \frac{dI(t)}{dt}, \hat{I}(t) = I_p e^{j(\omega t + \phi)}$$

$$\frac{dI(t)}{dt} = I_p j\omega e^{j(\omega t + \phi)} = j\omega I(t)$$

$$V(t) = L j\omega I(t)$$

$$\hat{Z}_L = \frac{\hat{V}(t)}{\hat{I}(t)} = jL\omega$$

RC Circuit w/ trig

KVL: $V_{in} = \frac{Q}{C} + IR \rightarrow \frac{dV_{in}}{dt} = R \frac{dI}{dt} + \frac{dQ}{dt}$ plug eq's in above

(1) $V_p \cos(\omega t) = R \omega I_p (\cos(\omega t + \phi) + \frac{1}{C} \sin(\omega t + \phi)) \rightarrow$ Isolate I_p, ϕ using

$$(\cos\phi + \frac{1}{\omega C} \sin\phi - \frac{V_p}{I_p R}) \cos(\omega t) + [-\sin\phi + \frac{1}{\omega C} \cos\phi] \sin(\omega t) = 0$$

$$\omega t = \frac{\pi}{2} \quad -\sin\phi + \frac{1}{\omega C} \cos\phi = 0$$

$$\tan\phi = \frac{1}{\omega C}$$

$$V_{in} = V_p \sin(\omega t)$$

$$I = I_p \sin(\omega t + \phi)$$

Caution don't do this way

$$\sin(\omega t + \phi) = \sin(\omega t) \cos\phi + \cos(\omega t) \sin\phi$$

$$\cos(\omega t + \phi) = \cos(\omega t) \cos\phi - \sin(\omega t) \sin\phi$$

valid for all this

use right triangle

ALG EBR finally some time

w/ trig

$$I_p = \frac{wCV_p}{\sqrt{1 + (\omega C)^2}}$$

$$I = \frac{wCV_p}{\sqrt{1 + (\omega C)^2}} \sin(\omega t + \phi), \phi = \tan^{-1}(\frac{1}{\omega C})$$

→ could use $\cos\phi = \frac{\cos\theta}{2}$ but that would be harder than trig

→ but $\text{Re}(e^{j\theta}) = \cos\theta$ is MUCH EASIER, on back.

make not
↓ take

$$e^{j\theta} = \cos \theta + j \sin \theta, |z| = 1 \Rightarrow e^{j\theta}$$

RLC w/ complex

KVL: $R \frac{dI}{dt} + \frac{I}{L} = \frac{dV_{in}}{dt}$

this step is semi
illegal, but works
out regardless you
would hold onto the
real part constants

$$V_{in} = V_p \cos(\omega t) = \operatorname{Re}(V_p e^{j\omega t})$$

$$I = I_p \cos(\omega t + \phi) = \operatorname{Re}(I_p e^{j(\omega t + \phi)}) = \operatorname{Re}(I_p e^{j\omega t})$$

[plug V_{in}, I into KVL] $\rightarrow R \hat{I}_p j\omega e^{j\omega t} + \frac{1}{L} \hat{I}_p e^{j\omega t} = j\omega V_p e^{j\omega t} \Rightarrow R \hat{I}_p j\omega + \frac{1}{L} \hat{I}_p = j\omega V_p$ (from L)

$$\hat{I}_p = \frac{\omega C V_p}{\omega RC - j\frac{1}{L}} \quad \begin{matrix} z = a + jb \\ a = \omega RC \end{matrix} \quad b = -1 \quad \tan \theta = -\frac{1}{\omega RC}$$

↓ then $\hat{I}_p = \frac{\omega C V_p}{(\omega RC)^2 + 1} e^{j\theta} \rightarrow I = \operatorname{Re}(\hat{I}_p e^{j\omega t}) = \operatorname{Re}\left[\frac{\omega C V_p}{(\omega RC)^2 + 1} e^{-j\theta} e^{j\omega t}\right] = \frac{\omega C V_p}{(\omega RC)^2 + 1} \operatorname{Re}(e^{j(\omega t - \theta)})$

$$I = \frac{\omega C V_p}{(\omega RC)^2 + 1} \cos(\omega t - \theta), \tan \theta = -\frac{1}{\omega RC}$$

* different from trig b/c cosine

GENERALIZATIONS

Real part of complex impedance \rightarrow resistance

Complex part of complex impedance \rightarrow reactance (X)

Generalized complex Ohms law: $\hat{V} = \hat{I} \hat{Z}$ b/c of how we define \hat{Z} .

$$\hat{Z} = R + jX = |Z| e^{j\theta} \quad \theta = \tan^{-1}\left(\frac{X}{R}\right), R = |Z| \cos(\theta), X = |Z| \sin(\theta)$$

$$\hat{Z}_{\text{series}} = \sum_i \hat{Z}_i$$

$$\frac{1}{\hat{Z}_{\text{parallel}}} = \sum_i \frac{1}{\hat{Z}_i}$$

Steps for any circuit:

$$1. \hat{V} = \hat{I} \hat{Z} \text{ (all complex)}$$

2. find \hat{Z}_{tot}

$$3. \text{ calculate } \hat{I} = \frac{\hat{V}}{\hat{Z}_{\text{tot}}}$$

$$4. \text{ get in form } a + jb = \hat{z}$$

$$5. \text{ convert to } |z| e^{j\theta} = \hat{z}$$

6. plug in \hat{V}

7. take real part of \hat{I}

different than trig b/c this
is (its drive not size, if
you had size it's same $\sin(\omega t + \phi)$)

$$\sin(\theta) \leftrightarrow \sin(\omega t + \phi)$$

$$\theta = \tan^{-1}(-\frac{1}{\omega RC}) \leftrightarrow \phi = \tan^{-1}\left(\frac{1}{\omega RC}\right)$$

BC again

$$② Z_{\text{tot}} = R + j\omega C$$

$$③ \hat{I} = \hat{V} / (R + j\omega C)$$

$$④ \hat{I} = \frac{\omega C V_p}{\sqrt{(\omega RC)^2 + 1}} e^{j\theta} \text{ using } z \text{ components } \theta = \tan^{-1}\left(\frac{-1}{\omega RC}\right)$$

$$⑤ \hat{V} \text{ can be } \operatorname{Re}(V_p e^{j\omega t}), V_p \cos(\omega t), \text{ or } \operatorname{Im}(V_p e^{j\omega t}), \sin(\omega t)$$

$$\text{lets do } \cos \theta = \frac{\omega C V_p}{\sqrt{(\omega RC)^2 + 1}} e^{j(\omega t - \theta)}$$

$$\hat{I} = \frac{\omega C V_p}{\sqrt{(\omega RC)^2 + 1}}$$


$$⑦ I = \operatorname{Re}(\hat{I}) = \frac{\omega C V_p}{\sqrt{(\omega RC)^2 + 1}} \cos(\omega t - \theta), \tan \theta = \frac{-1}{\omega RC}$$

Bonus side note

• to get V_C , use $\frac{dQ}{dt} = I$ and integrate I then
divide by C , or shortcut $V_C = \frac{Q(t)}{C}$

• fancy this in RC circuit $\hat{V}_R = \frac{Z_R}{Z_R + Z_C} \hat{V}(t)$, voltage divider!

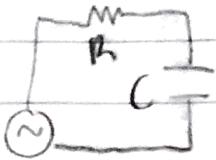RC circuit as differentiator and Integrator



$$\downarrow \hat{V}(t) = V_p e^{j\omega t}$$

differentiator

$$\rightarrow \text{if } |1/Z_R| \ll |Z_L| \text{ for } \hat{V}_R(t) \approx \hat{V}(t) \quad \frac{\hat{Z}_R}{\hat{Z}_L} = \hat{V}(t) j\omega R L$$

\rightarrow if you look at $dI(t) = j\omega \hat{V}(t)$, so if Z_R is very small you can use RL factor $j\omega L$ to differentiate.

$$\hat{V}_R(t) = \frac{d\hat{V}(t)}{dt} R L = \hat{V}(t) j\omega R L$$

$$\rightarrow \left(\frac{d\hat{V}(t)}{dt} = \frac{1}{RL} \hat{V}_R(t) \right)$$

Integrator

$$\rightarrow \text{if } |1/Z_R| \gg |Z_L| \quad \hat{V}_L(t) \approx \frac{\hat{Z}_L}{\hat{Z}_R} \hat{V}(t) = \hat{V}(t) \frac{1}{j\omega RL}$$

\rightarrow if you look at $\int \hat{V}(t) dt = \frac{1}{j\omega} \hat{V}(t)$ which is very similar to

$$\hat{V}_L(t) = \frac{1}{j\omega} \int \hat{V}(t) dt = \frac{1}{j\omega RL} \hat{V}(t)$$


$$\left(\int \hat{V}(t) dt = RL \hat{V}(t) \right)$$

High Pass/Low Pass filters

Low PASS:

$$|V_{out}| = \frac{|Z_L|}{|Z_R + Z_L|} |\hat{V}(t)| = \frac{V_p}{\sqrt{(\omega R)^2 + 1}} \quad (\text{no cos part})$$

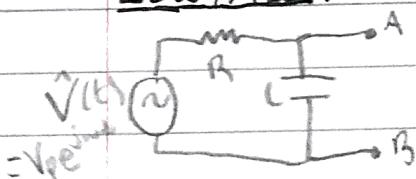
(just amplitude part)
↳ A $\cos(\omega t - \theta)$



$$\left[\begin{array}{l} \text{at } \omega \rightarrow 0, |V_{out}| = |V| \\ \text{at } \omega \rightarrow \infty, |V_{out}| \rightarrow 0 \end{array} \right]$$

so at low frequencies voltage is passed but at high it blocked

HIGH PASS

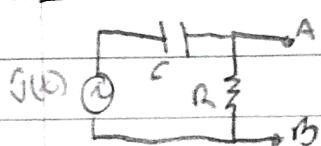


$$|V_{out}| = \frac{|Z_R|}{|Z_C + Z_R|} |\hat{V}(t)| = V_p \frac{R \omega}{\sqrt{(R \omega)^2 + 1}}$$

$$\left[\begin{array}{l} \omega \rightarrow 0, |V_{out}| = 0 \\ \omega \rightarrow \infty, |V_{out}| \rightarrow |V| \end{array} \right]$$


High frequency pass filter

$$T(\omega) = \frac{1}{\sqrt{2}} \text{ when you plug } \omega = \infty$$

low

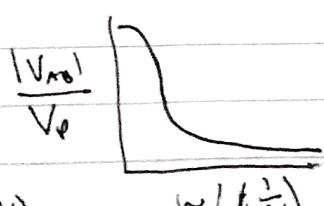

high

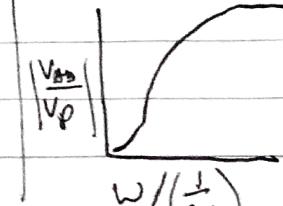

$$\text{Transmission: } T(\omega) = \frac{|V_{out}|}{|V_{in}|} = \frac{1}{\sqrt{(\omega R)^2 + 1}} = \frac{|V_{out}|}{|V_p|}$$

* just output voltage V_{out} w/ V_p (Amplitude)

$$\text{high: } T(\omega) = \frac{|V_{out}|}{|V_{in}|} = \frac{\omega R C}{\sqrt{(\omega R)^2 + 1}} = \frac{|V_{out}|}{|V_p|}$$

* output voltage is voltage divider (what's transmitted)


Decibels compares amplitudes:

$$\text{for } P_{avg} = A^2 / 2R = \frac{A_{rms}^2}{R}$$

$$dB = 20 \log_{10} \left(\frac{A_2}{A_1} \right) = 10 \log_{10} \left(\left(\frac{A_2}{A_1} \right)^2 \right) = 10 \log_{10} \left(\frac{P_2}{P_1} \right) \text{ other constants cancel}$$

(ex) if $A_2 = 2A_1$, then $\Rightarrow 20 \log(2) \approx 6$ so A_2 is 6 decibels higher

[what about
Inductors]

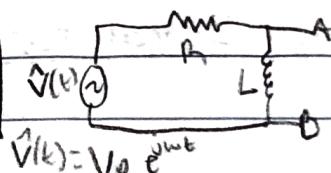


$$\hat{V}_{ab} = \hat{V}(t) \frac{\hat{Z}_L}{\hat{Z}_L + \hat{Z}_R} = \hat{V} \frac{j\omega L}{j\omega L + R}$$

$$\text{full detail: } \hat{V}_{ab} = \hat{V}(t) \frac{-\omega L}{Rj - \omega L}, \quad a = -\omega L \rightarrow \hat{V}_{ab} = \frac{-\omega L}{R^2 + (\omega L)^2} e^{j\omega t} V_p e^{-j\theta} = \frac{-V_p \omega L}{\sqrt{R^2 + (\omega L)^2}} e^{j(\omega t - \theta)}$$

$$\text{Re}(\hat{V}_{ab}) = \frac{-V_p \omega L}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t - \theta), \text{ let's look at amplitude:}$$

$$T = \frac{V_{ab}}{V_p} = \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}} \quad [w \rightarrow 0, T=0, w \rightarrow \infty, T \rightarrow 1] \quad (\text{High Pass})$$

[Band Pass
Filters]

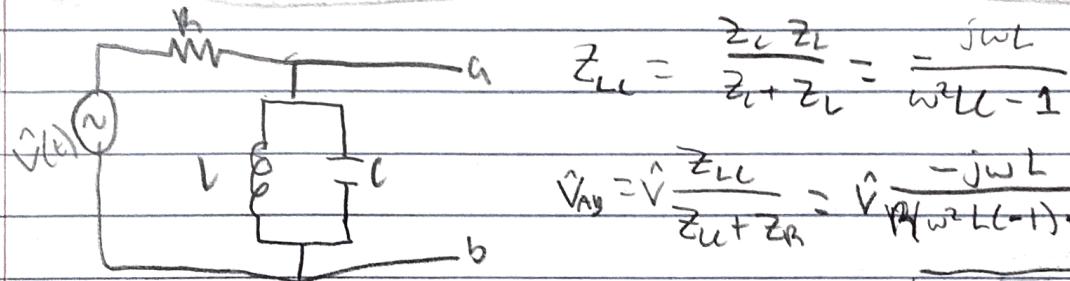

$$Z_{LC} = \frac{Z_L Z_C}{Z_L + Z_C} = \frac{j\omega L}{\omega^2 LC - 1}$$

$$\hat{V}_{ab} = \hat{V} \frac{Z_{LC}}{Z_R + Z_{LC}} = \hat{V} \frac{-j\omega L}{R^2(\omega^2 LC - 1) + j\omega L}$$

Both 0!

$$\text{Convert to Real } T = \frac{V_{ab}}{V_p} = \frac{\omega L}{\sqrt{R^2(\omega^2 LC - 1)^2 + (\omega L)^2}} \quad [w=0 \quad T=0]$$


look at ratio of A

$$\rightarrow \text{if you do } \frac{dT}{dw} = 0 \rightarrow w_o = \sqrt{\frac{1}{LC}} = \sqrt{\frac{R}{L} \cdot \frac{1}{R_C}} \text{ and } \frac{R}{L} = w \text{ for inductor, } \frac{1}{R_C} = w \text{ for capacitor}$$

High pass low pass

$$\text{Band width} = \Delta w = w_C - w_L$$

[Notch
Filter]

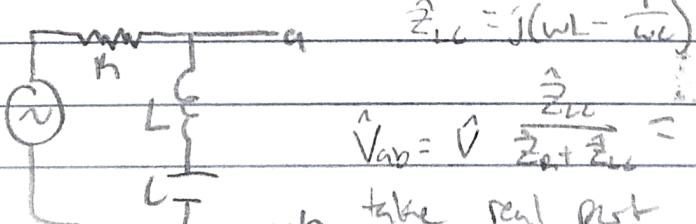

$$Z_{LC} = j(wL - \frac{1}{wC})$$

$$\hat{V}_{ab} = \hat{V} \frac{Z_{LC}}{Z_R + Z_{LC}} = \hat{V} \frac{j(w^2 LC - 1)}{R^2 w^2 LC + j(w^2 LC - 1)}$$


take real part & look at amplitude ratio

$$T = \left| \frac{V_{ab}}{V_p} \right| = \left| \frac{w^2 LC - 1}{\sqrt{(R^2 w^2)^2 + (w^2 LC - 1)^2}} \right| \quad [w=0 \quad T=1]$$

$$[w=\infty \quad T=1]$$

$$\text{0 happens at } w = \frac{1}{\sqrt{LC}} = w_0 = \sqrt{w_L \cdot w_C} \text{ capacity}$$

$$w_0$$

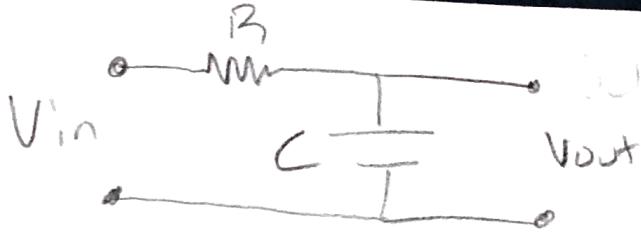

RLC circuits Part 2

(Capacitor charging and discharging unified)

$$\text{AVL: } V_{in} - \frac{q}{C} - \frac{dq}{dt} R = 0 \Rightarrow V_{in} = \frac{q}{C} + \frac{dq}{dt} R$$

general sol'n: $q = A e^{-t/\tau_{RC}} + B$ and $V_C = \frac{q}{C}$
 C is constant so $\frac{A}{C} = a$

$$V_C = a e^{-t/\tau_{RC}} + b$$

$V(t=0) = V_{initial}$ and $V(t=\infty) = V_{final}$

$a+b = V_{initial}$ $b = V_{final}$

$$a = V_{initial} - V_{final} = -\Delta V$$

$$V_C = V_{final} - \Delta V e^{-t/\tau_{RC}}$$

V_{final} is source voltage after switching
 Meaning the capacitor's final voltage
 By the source

RC circuits as integrator

$$V_{in} - V_R - V_C = 0 \text{ and } V_R = I R \Rightarrow I = \frac{V_R}{R} = \frac{V_{in} - V_C}{R}, V_C = \frac{q}{C} = \frac{1}{C} \int I dt$$

$$V_C = \frac{1}{C} \int I dt = \frac{1}{C} \int \frac{V_{in} - V_C}{R} dt \quad \begin{array}{l} \text{and it there} \\ \rightarrow \text{is any initial} \\ \text{voltage} \end{array} \quad V_C = V_{initial} + \frac{1}{C} \int I dt$$

for any circuit

$$\hat{V} = \hat{I} \hat{Z} \quad (\text{complex ohm's law})$$

Find \hat{Z}_{tot}

$$\text{calculable } \hat{I} = \frac{\hat{V}}{\hat{Z}_{tot}}$$

get in form $a + jb$

convert complex to real

$$1 \hat{I} e^{j\theta}$$

take real part

ex) RC circuit:

$$(2) \hat{Z}_{tot} = R + j\omega C$$

$$(3) \hat{I} = \frac{\hat{V}}{R + j\omega C}$$

$$(4) \hat{I} = \frac{\omega C \hat{V}}{\sqrt{(\omega RC)^2 + 1}} e^{j\theta}, \text{ using } |z| \rightarrow \tan \theta = \left(\frac{-1}{\omega RC} \right)$$

ALTERNATING Current

5) for \hat{V} can be either $V_p \cos(\omega t)$ or $V_p \sin(\omega t)$

either case we can use $V_p e^{j\omega t}$ with the previous

that at the end we will take real part for cosine drive

or Imaginary part for sin drive


$$\hat{I} = \frac{\omega C V_p}{\sqrt{(\omega RC)^2 + 1}} e^{j(\omega t - \theta)}$$

$$(6) I = \text{Re}(\hat{I}) = \sqrt{(\omega RC)^2 + 1} \cos(\omega t - \theta)$$

Big side note: when taking Im part your answer will look a lot different from the trig value on book. $\Theta = \tan^{-1}(\frac{1}{\omega RC})$ vs $\Theta = \tan^{-1}(\frac{1}{\omega RC})$

Book notes

RC circuit Response to a Sine Wave

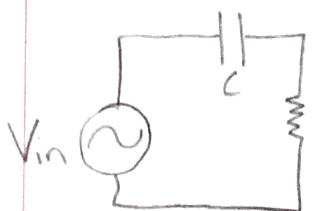

$$KVL: V_{in} = \frac{Q}{C} + IR$$

$$\left[\text{take derivative} \right] \frac{dV_{in}}{dt} = R \frac{dI}{dt} + \frac{I}{C} \quad (1)$$

not $\neq 0$ b/c voltage isn't constant

essentially
current diff eq
by unit step
and previous
right answer

- $V_{in} = V_p \sin(\omega t)$, V_p is amplitude sin is changing w/t time,

- assume current follows same sinusoidal pattern

$$I = I_p \sin(\omega t + \phi), I_p, \phi \text{ are constants to be determined}$$

$$\text{plugging into (1)} \rightarrow \omega V_p \cos(\omega t) = R \omega I_p \cos(\omega t + \phi) + \frac{I_p}{C} \sin(\omega t + \phi)$$

taked dt where ness

$$\text{isolating } I_p, \phi \left[\sin(\omega t + \phi) = \sin(\omega t) \cos(\phi) + \cos(\omega t) \sin(\phi) \right] \left\{ \begin{array}{l} \text{now divide by } R \omega I_p \text{ and} \\ \text{apply the identities} \end{array} \right\}$$

$$\text{trig identities: } (\cos(\omega t + \phi) = \cos(\omega t) \cos(\phi) - \sin(\omega t) \sin(\phi))$$

$$\hookrightarrow (\cos(\omega t) \cos(\phi) - \sin(\omega t) \sin(\phi)) + \frac{1}{wRC} (\sin(\omega t) \cos(\phi) + \cos(\omega t) \sin(\phi)) = \frac{V_p}{I_p R} \cos(\omega t)$$

$$\hookrightarrow \left[\cos\phi + \frac{1}{wRC} \sin\phi - \frac{V_p}{I_p R} \right] \cos(\omega t) + \left[-\sin\phi + \frac{1}{wRC} \cos\phi \right] \sin(\omega t) = 0$$

this is valid for all times so lets choose some that's convenient

$$t=0: \cos\phi + \frac{1}{wRC} \sin\phi - \frac{V_p}{I_p R} = 0 \quad \left[\omega t = \frac{\pi}{2} \right]: -\sin\phi + \frac{1}{wRC} \cos\phi = 0$$

Using right triangle:

$$\sin\phi = \frac{1}{\sqrt{1 + (wRC)^2}}, \cos\phi = \frac{wRC}{\sqrt{1 + (wRC)^2}}$$

Using these yields

$$\frac{wRC}{\sqrt{1 + (wRC)^2}} + \frac{1}{wRC}, \frac{1}{\sqrt{1 + (wRC)^2}} = \frac{V_p}{I_p R} \quad \left[\begin{array}{c} A \\ L \\ G \\ F \\ B \end{array} \right] \Rightarrow I_p = \frac{\omega t}{\sqrt{1 + (wRC)^2}} V_p$$

Thus the final sol'n

$$\rightarrow I = \frac{\omega C V_p}{1 + (wRC)^2} \sin(\omega t + \phi), \phi = \tan^{-1}\left(\frac{1}{wRC}\right)$$

$$R \frac{dI}{dt} + \frac{I}{C} = \frac{dV_{in}}{dt}, \left\{ \begin{array}{l} I = I_p \cos(\omega t + \phi) = \operatorname{Re}(I_p e^{j(\omega t + \phi)}) = \operatorname{Re}(I_p e^{j\omega t}), I = \text{complex current amplitude?} \\ V_{in} = V_p \cos(\omega t + \phi) = \operatorname{Re}(V_p e^{j\omega t}) \end{array} \right.$$

$$I_p e^{j\phi} = I_p \quad \text{a nice substitution}$$

$$\text{Plug in: } R \hat{I}_p j\omega C + \frac{1}{C} \hat{I}_p = j\omega V_p e^{j\omega t} \Rightarrow R \hat{I}_p j\omega + \frac{1}{C} \hat{I}_p = j\omega V_p \quad [\text{solve for } \hat{I}_p]$$

$$\hat{I}_p = \frac{\omega C V_p}{wRC - j} \quad \left\{ \begin{array}{l} \hat{z} = [a + bi] \\ a = wRC \\ b = -1 \\ |z| = \sqrt{a^2 + b^2} = \sqrt{wRC} \end{array} \right. \quad \left\{ \begin{array}{l} |\hat{z}| = \sqrt{(wRC)^2 + (-1)^2} \\ \hat{z} = \sqrt{(wRC)^2 + 1} e^{j\theta} \end{array} \right. \quad \left\{ \begin{array}{l} \hat{I}_p = \frac{\omega C V_p}{\sqrt{(wRC)^2 + 1}} e^{-j\theta} \end{array} \right.$$

take the Re part

$$\text{Now take "real part"} \rightarrow I = \operatorname{Re}[\hat{I}_p e^{j\omega t}] = \operatorname{Re}\left[\frac{\omega C V_p}{\sqrt{(wRC)^2 + 1}} e^{-j\theta} e^{j\omega t}\right] = \frac{\omega C V_p}{\sqrt{(wRC)^2 + 1}} e^{j(\omega t - \theta)}$$

$$\text{original: } I = I_p \cos(\omega t + \phi)$$

$$\text{answer: } I = \frac{\omega C V_p}{\sqrt{(wRC)^2 + 1}} \operatorname{Re}(e^{j(\omega t - \theta)})$$


$$\text{rec: } I_p \operatorname{Re}(e^{j(\omega t - \theta)}) = I_p (\cos\omega t - \theta)$$

$$\operatorname{Re}(e^{j\theta}) = \frac{e^{j\theta} + \bar{e}^{j\theta}}{2}$$

$$\operatorname{tans} = -\frac{1}{wRC}$$


so
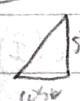
$$I = \frac{\omega C V_p}{\sqrt{(wRC)^2 + 1}} (\cos(\omega t - \theta))$$



$$\begin{aligned} e^{j\theta} &= (\omega t - j\theta) \\ \text{take real part proj on Re axis} \\ \operatorname{Re}(e^{j\theta}) &= \cos\theta + j\sin\theta \end{aligned}$$

Transformers

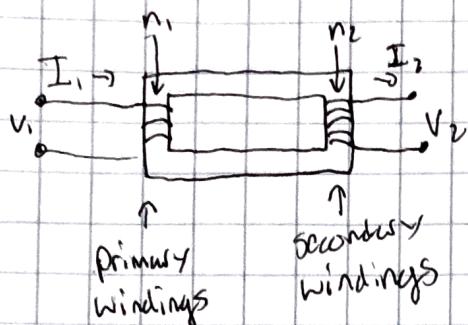

→ Faraday's law states that a time varying magnetic field inside of a coil of wire induces a voltage this voltage is V_2

$$\text{equation is } \underline{V_2 = \left(\frac{N_2}{N_1}\right)V_1}$$

(if a resistor) (to the secondary)
(or another load) (coil a current
(is attached) (I2 can flow)

flipped so if $\uparrow V$ then
energy has to be cons.

$$I_2 = \left(\frac{N_1}{N_2}\right) I_1$$

"turns ratio"

Impedance matching

{ Voltage source = V_0
internal resistance = R_0

connect to load resistor = R_L

form law w/ total \rightarrow how should R_0 and R_L
be related if we want max power
to the load resistor

$$P_L = I^2 R_L = \left(\frac{V_0}{R_0 + R_L}\right)^2 R_L$$

{ pretty much trying to find right balance of I and V to max
power, balance happens when $R_L = R_0$ }

To find extrema: $\frac{dP_L}{dR_L} = V_0^2 \left[\frac{1}{(R_0 + R_L)^2} - \frac{2R_L}{(R_0 + R_L)^3} \right] = 0$

you get $R_L = R_0$ for
max power transfer

[source resistance must match load]


BUT not everything will have that desired resistance so to match impedance we use transformers.

$$V_2 = I_2 R_L \rightarrow V_1 \left(\frac{N_2}{N_1}\right) = I_1 \left(\frac{N_1}{N_2}\right) R_L \rightarrow V_1 = I_1 \left[\left(\frac{N_1}{N_2}\right)^2 R_L\right]$$

which also shows $\frac{V_1}{I_1} = R_{eff} = \left(\frac{N_1}{N_2}\right)^2 R_L$

so what was R_L before
is now R_{eff}

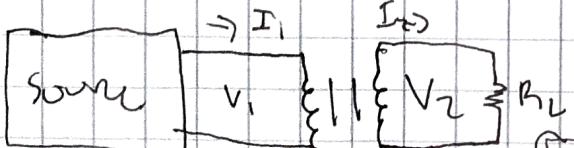The point is the transformer has changed the resistance the source "sees" from R_L to R_{eff} . By choosing a transformer w/ correct N_1/N_2 you can match R_{eff} to whatever source resistance you have, insuring max power.



Source produces current & has an

loss resistance, source carries current & voltage

by Faraday's law. We can't change the windings to match to R_L


this is ideal case
but $R_0 \neq R_L$ always
equal R_0 , so we use

transformers,

Power lost due to resistance by source

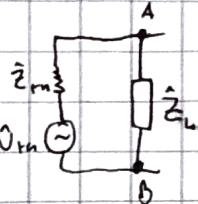
Example

Before we were power impedance matching but there's voltage impedance matching (give smaller answer)



$$V_{out} = V_{oc} \left(\frac{Z_L}{Z_L + Z_m} \right)$$

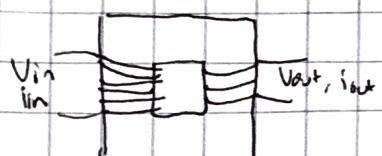[in order for V_{oc} to be delivered to Z_L , $Z_L > Z_m$, if Z_L is too small the source gets too much voltage, so we use transformer]



$$\frac{V_{out}}{V_{in}} = \frac{N_{out}}{N_{in}}$$

$$Z_{in} = \frac{V_{in}}{I_{in}}, Z_{out} = \frac{V_{out}}{I_{out}}, \frac{Z_{out}}{Z_{in}} = \frac{V_{out}^2}{V_{in}^2} = \left(\frac{N_{out}}{N_{in}} \right)^2$$

$$V_{in} I_{in} = V_{out} I_{out}$$



An audio source has an output impedance of 200Ω. Design a filter that Transmits more than 90% of frequencies above 15 kHz but less than 10% of frequency below 2 kHz.


$$T = \frac{R_{wc}}{\sqrt{(R_{wc})^2 + 1}} \quad R_{wc} = 2 \text{ k}\Omega \quad T = .9 \text{ @ } 15 \text{ kHz} \rightarrow C = 1.1 \cdot 10^{-8} = 11 \text{ nF}$$

$$T = \frac{1}{\sqrt{1 + (R_{wc}/T)^2}} \quad \rightarrow \text{plug in } T = .1 \text{ @ } 2 \text{ kHz} \rightarrow C = 4.0 \cdot 10^{-8} = 40 \text{ nF}$$

$\rightarrow R$ should be 10·R_{wc} and $T > 90\%$ at 15 kHz, $T < 10\%$ at 2 kHz

$\rightarrow T$ for a high pass filter

Theorem AC

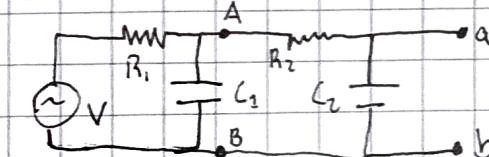

$$V_{AB} = ? \quad (V_{AB} = V_{oc} \text{ in this case})$$

$$|V_{AB}| = \left| \frac{Z_{c1}}{Z_m + Z_{c1}} \right| |V| = \frac{|V_p|}{\sqrt{(R_{m2}Y_{m1})^2 + |Z_{m1}|^2}} \quad \frac{R_1 \left(\frac{-j}{\omega C_1} \right)}{R_1 - \frac{j}{\omega C_1}} = \frac{R_1}{\sqrt{(R_{m2}Y_{m1})^2 + 1}}$$

$$|V_{ab}| = |V_{AB}| \left| \frac{R_{c2}}{R_{c2} + (A_{m1} + R_2)} \right|$$

$$|B_{m2}| = \frac{(R_2 + B_m) Z_{c2}}{Z_{c2} + Z_m + Z_{c1}}$$

{ If this varies in time it can make shapes! }

Lissajous patterns

for our voltage signals you can look at inductor patterning

$$y_1 + y_2 = \cos\left(\frac{2\pi t}{T}\right) + \cos\left(\frac{2\pi t}{T} + \phi\right) \\ = 2\cos\left(\frac{\pi t}{T} + \frac{\phi}{2}\right)\cos\left(\frac{\phi}{2}\right)$$

- take our "cos" signal

$$y_1 = \cos(\omega t) \quad \leftarrow \text{this could be like voltage sign, you could plot it like } y_1$$

$$y_2 = \cos(\omega t + \phi) \quad \leftarrow \text{this could be like current, here it's like } y_2$$

$$\text{ex. } \phi = 0$$




$$y_1 = \cos(\omega t)$$

$$y_2 = \cos(\omega t + 0)$$


$$\phi = 90^\circ$$

$$y_1 = \cos(\omega t)$$
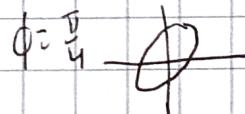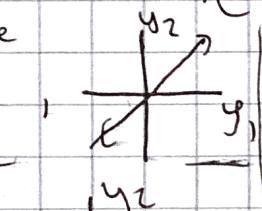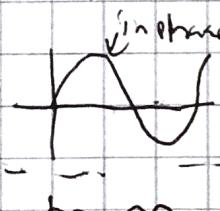
$$y_2 = \cos(\omega t + 90^\circ) = \sin(\omega t)$$



for different frequency

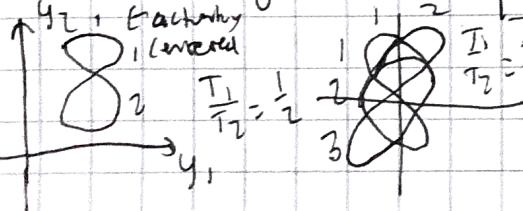

$$I_1 = \frac{2}{3}, I_2 = \frac{1}{3}$$

$$T_1 = \frac{N_1}{N_2} \text{ & number of x-axis long.}$$

$$T_2 = \frac{N_2}{N_1} \text{ & number of vertical y-axis long.}$$