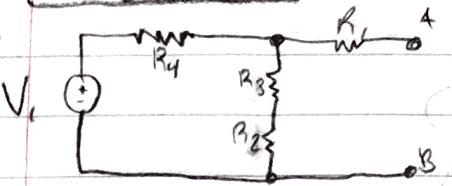


Thevenin Break down simple examples

Voltage divider

(1)



$$\text{KVL: } V_1 - I(R_2 + R_3 + R_4) = 0 \text{ and } V_{AB} - I(R_2 + R_3) = 0$$


No voltage (replace source w/ wire and connect AB)

$$\Rightarrow R_{th} = \frac{(R_2 + R_3) R_4}{(R_2 + R_3) R_4 + R_1}$$

$$\text{And } V_{AB} = V_{th} = \frac{(R_2 + R_3)}{(R_2 + R_3 + R_4)} V_1$$


no resistor here what will be difference?

(2)

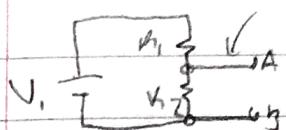

$$\text{No current: } V_{AB} = V_{th} = V_1 \left(\frac{R_2}{R_1 + R_2} \right)$$


No voltage:

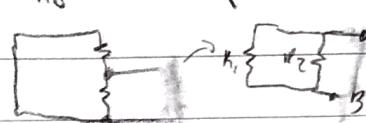

$$R_{th} = R_2 + R_3$$


or find I_{SC} . $V_1 \xrightarrow{R_2} R_3 \xrightarrow{I_{SC}} R_2$ won't go to the so $V_1 = I_{SC} R_2 \Rightarrow I_{SC} = \frac{V_1}{R_2}$
then use $V_{th} = I_{SC} R_{th}$

Bridger difference

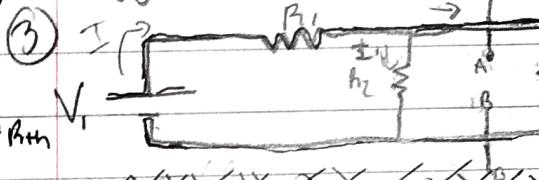

All these are legal.

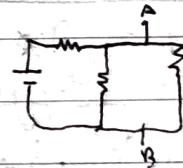(1) find V_{AB} , which is the drop across R_3 if you just follow the wire or do



~~$V_{AB} = R_3 / (R_1 + R_2 + R_3) V_1$ have to find $R_1 + R_2 + R_3$~~ ~~so $V_{AB} = R_3 / (R_1 + R_2 + R_3) V_1$~~


~~JUST USE KVL~~

DON'T
USE
 $V_1 - I_B R_1 - I_A R_2 = 0$

$$V_1 - I_B R_1 - I_A R_2 = 0 \Rightarrow V_{AB} = V_1 - I_B R_1$$

could use simplified loop to plug into I

but voltage divider eq is much easier!

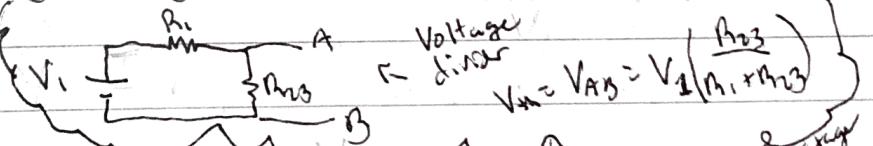

$$V_{th} = V_{AB} = V_1 \left(\frac{R_2}{R_1 + R_2} \right)$$

notice its a voltage divider w/ or parallel

Quick Recap of Voltage divider



- 1) $V_{in} - I(R_1 + R_2) = 0$
- 2) $V_{AB} = I(R_2) = 0$

* plug I into an eq & solve for V_{AB} no current through R_1

$$V_{AB} = V_{in} \left(\frac{R_2}{R_1 + R_2} \right)$$

$$R_{eq} = \frac{1}{R_2} + \frac{1}{R_{in}}$$

as $R_{in} \rightarrow \infty$


$$R_{eq} \rightarrow R_2$$

so you want voltage to have a high R

Input Resistance

- the measuring instrument becomes part of the circuit

(ex)

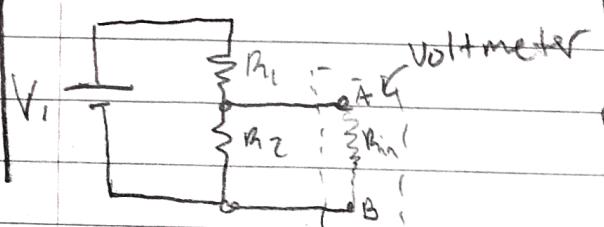

ignore R_{in} and Voltmeter for a sec its voltage divider so!

$$V_{AB} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) \quad (1)$$


this is what the meter will read at

- But since it's not a perfect voltmeter it has a R_{in}
- R_2 and R_{in} are in series so:

$$R_{net} = \frac{R_{in} \cdot R_2}{R_2 + R_{in}} \rightarrow \text{Plug this into (1) b/c its its eq Resistance between } R_{in} \text{ and } R_2$$

$$\rightarrow V_{AB} = V_1 \left(\frac{(R_{in} \cdot R_2)}{R_2 + R_{in}} \right) \parallel \frac{R_2}{R_2 + R_{in}} = R_{in}(R_{in} + R_2) + R_2 R_{in}$$

cascade of Thevenin's

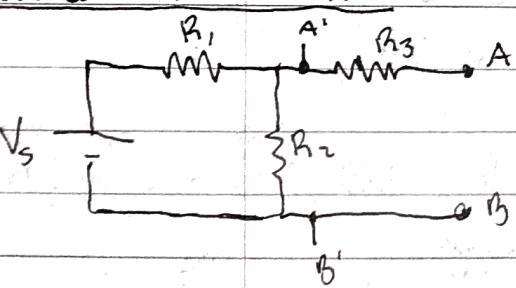

$$(1) V_{A'B'} = V_{oc} = V_s \frac{R_2}{R_1 + R_2}$$

If you ignore R_3 and V_{AB}

you can see $A' B'$, $V_{A'B'}$ is just a voltage divider so we can use Thevenin to simplify the left,

(for 1stn replace V_s w/ V_{th})

$$R_{th} = R_1 \parallel R_2 \text{ so } R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$







$$R_{th} = R_3 + R_4$$

→ since there's no current and

subsequently no drops across $V_{th} + R_4$


$$V_{th} = V_{th}$$

how to do R_{th} for Wheatstone:

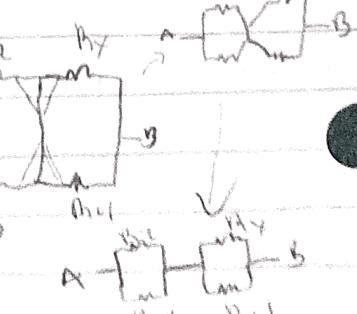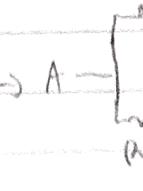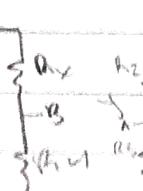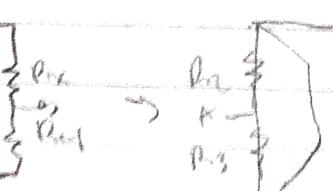

Diodes in Circuits • an ideal diode has $Z = \infty$ when $V < 0$ and $Z = 0$ when $V > 0$

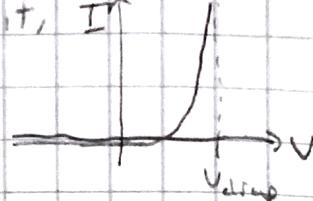• a real diode has a V_{drop} across it, $I \uparrow$



6

$$\text{Shockley diode eq'n: } I = I_0 [e^{\frac{eV}{kT}} - 1]$$

easy approximation: if $V \gg V_{drop}$ \rightarrow if $V < V_{drop}$, $I = 0$

if $V_{drop} \gg V$ \rightarrow if $V \geq V_{drop}$: KVL $V = V_{drop} - IR \Rightarrow I = \frac{V_o - V_{drop}}{R}$

(If we use Schokley) $\rightarrow V_o - IR - V_d = 0 \rightarrow I \cdot \frac{V_o - V_d}{R} = I_0 (e^{\frac{eV_d}{kT}} - 1)$





*Solve w/ Newton's method or "load line"

(origin of
Voltage vs
equations I
don't understand)

$$I = I_0 e^{\frac{eV}{kT}} [e^{\frac{eV}{kT}} - 1], \text{ when } \frac{eV}{kT} \gg 1, \frac{k_B T}{e} (\ln I - \ln I_0) = V - \frac{\Delta E}{e}$$


this is V_d ? energy diagram

Making an AC oscillator

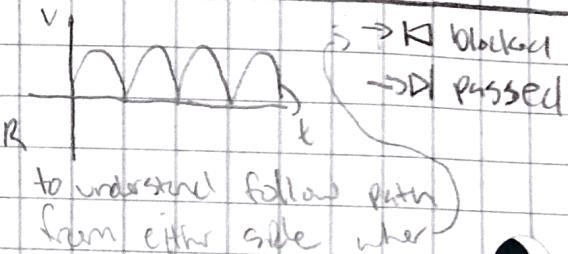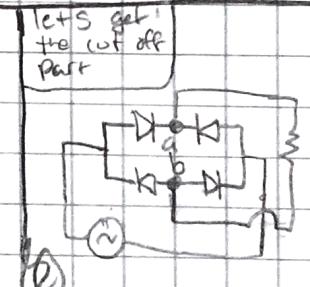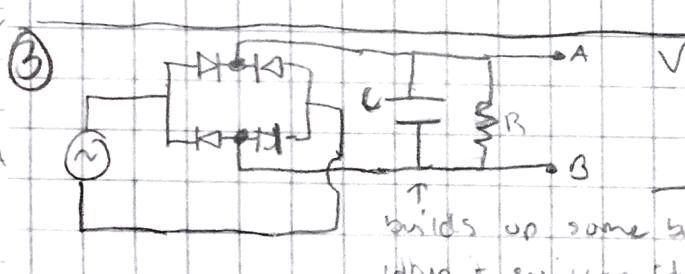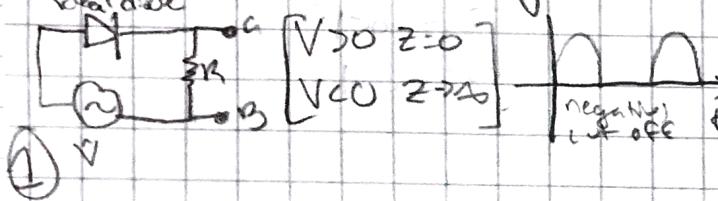

②

③

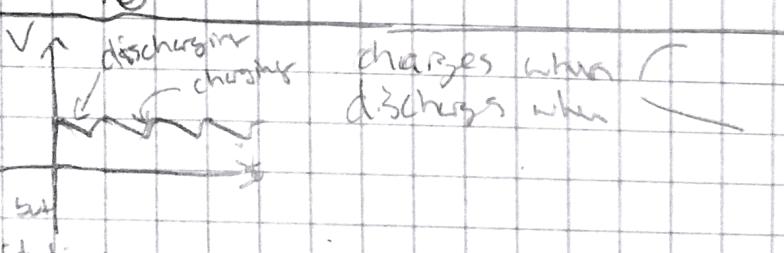

→ this is one way to filter out the signals.

But what is actually happening?


At certain times the capacitor is \rightarrow you don't want it to charge quickly, to do this, you need

✓ input port

- high capacitance

- C be high? so it acts like wire or doesn't conduct much

- how $f_C = 1/\pi RC$

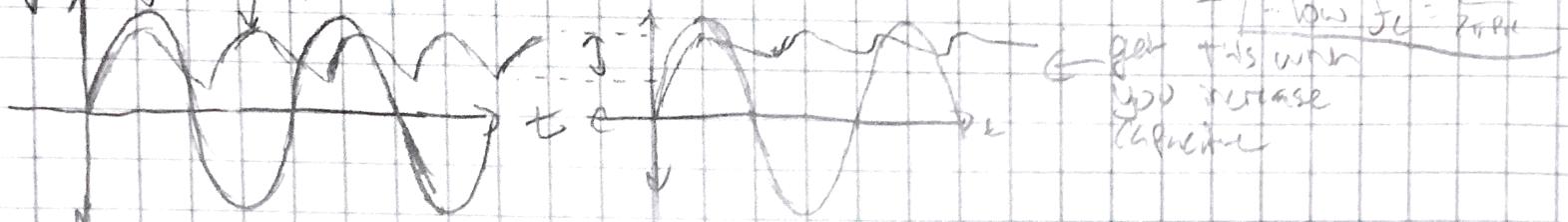

Ripple factor of circuit?

form factor?


\downarrow Voltage (rms) of output signal = $V_{\text{rms(AC)}} \leftarrow \text{"AC part"}$

Γ : Average value of signal = $V_{\text{DC}} \leftarrow \text{"direct current part"}$

[getting equations]

$$P = \frac{1}{T} \int \frac{V(t)^2}{R} dt = \frac{V_{\text{rms}}^2}{R}$$
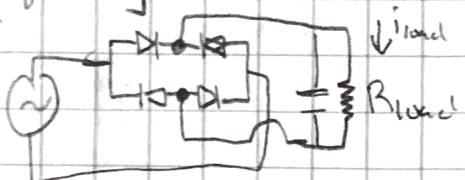
$$\Rightarrow V_{\text{rms}}^2 = \frac{1}{T} \int_0^T V(t)^2 dt$$



$$V_{\text{DC}} = \frac{1}{T} \int_0^T v(t) dt$$

usually output
Voltage V_{DC} or
V_{load}

of the load

* you can say: $C_L(t) = \frac{V_L(t)}{R_L}$ and $I_{\text{DC}} = \frac{V_{\text{DC}}}{R_L}$ and $I_{\text{rms}} = \frac{V_{\text{rms}}}{R_L}$

Lets think about DV drop of the capacitor that's causing these ripples

[for small ripples]

[you can approximate]

[I want to be constant]

$$\begin{cases} Q = CV \\ I = C \frac{dV}{dt} \end{cases}$$

$$\Rightarrow \Delta V = \frac{I}{C} \Delta t$$

$\Delta t \approx \frac{T}{2}$ (half wave rectifier)

$\Delta t \approx \frac{1}{2f}$ (full wave rectification)

* resistor causes capacitor to discharge "somewhat" between cycles (or half cycles for full wave rectification)



[assuming a linear approximation it is conservative in design]

$$\Delta V = \frac{I_{\text{load}}}{fC} \quad \text{or} \quad \Delta V = \frac{I_{\text{load}}}{2fC}$$



* I think I_{load} is current across the diodes DCC/

the resistor is what is making its $\frac{dV}{dt}$

↳ can't discharge anywhere else

Spec in
V_{CC} gives we
Broad
care about


Zener diode
Practice Problems

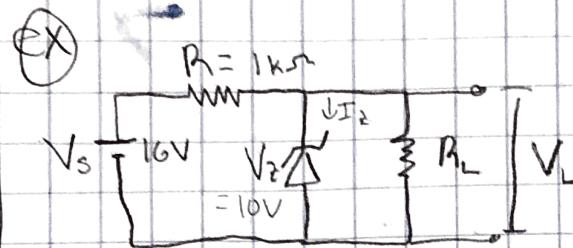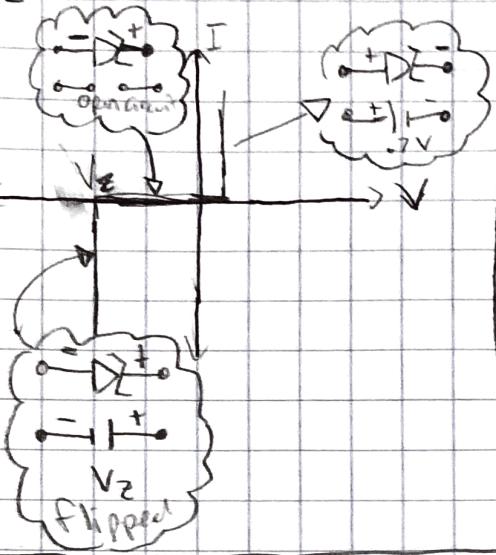

8

$R_L = 1.2 \text{ k}\Omega$; find state of zener diode by seeing voltage V_L .
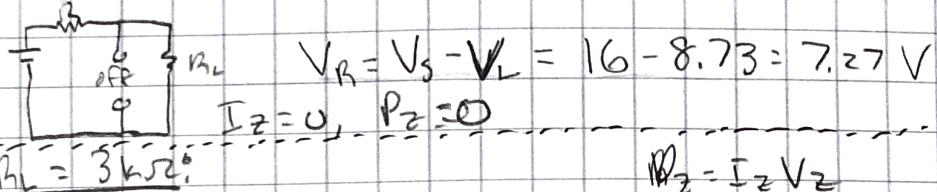
$$V_L = V_Z = V_s \frac{R_L}{R_L + R} = 8.73 \text{ V} \text{ so zener is OFF}$$



$$V_L = V_{\text{Zener}} = V_s \frac{R_L}{R_L + R} = 12 \text{ V} \text{ so zener on}$$

$$V_{\text{Zener}} = V_L = 10 \text{ V} \quad (\text{Zener regulates voltage})$$

$$V_R = V_s - V_L = 16 - 10 = 6 \quad | \quad I_L = \frac{V_R}{R_L} = \frac{10}{3 \text{ k}\Omega} = 3.33 \text{ mA}$$

$$I_R = \frac{V_L}{R_L} = 6 \text{ mA} \quad | \quad I_Z = I_R - I_L = 6 - 3.33 = 2.67 \text{ mA}$$

To find the minimum load resistance such that
(if $R_L > R_{\text{min}}$, Zener is on and $R_L < R_{\text{min}}$ Zener is off)

$$\hookrightarrow \text{Also } I_{L\text{max}} = \frac{V_L}{R_L} = \frac{V_Z}{R_{\text{min}}}$$


Since Zener diode regulates, there is a max resistance, (has an I_{Zm} where it breaks down)

Once the diode is on $I_Z = I_R - I_L$ (I_Z is limited to I_{Zm}) $\rightarrow I_{Zm} = I_R - I_{L\text{min}}$

$$\text{Generally: } R_L = \frac{V_L}{I_L} \Rightarrow R_{\text{min}} = \frac{V_Z}{I_{R\text{min}}} = \frac{V_Z}{I_R - I_{Zm}}$$

So Zener is on when: $I_{L\text{min}} < I_L < I_{R\text{max}}$, $R_{\text{min}} < R_L < R_{\text{max}}$

Transistor example problems

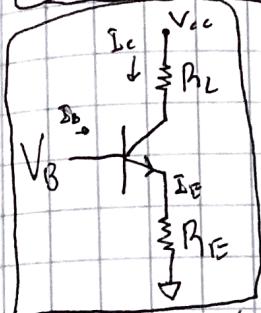

BE loop

$$V_B = V_{BE} + I_E R_E$$

* if transistor is conducting then $V_{BE} = V_{drop}$

$$\Rightarrow V_B = V_{drop} + I_E R_E$$


(think discrete levels)

$$I_C = \beta I_B \quad (\text{only true for linear active region}) \quad \text{then } I_C = \frac{\beta}{1+\beta} I_E \approx I_E$$

then

$$I_C \approx I_E = \frac{V_B - V_{drop}}{R_E}$$

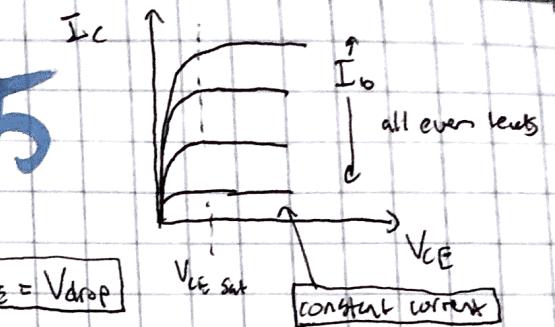* I_C is controlled by V_B , doesn't depend on load *
(current source b/c its constant and doesn't change)



5

Q1 Given R_E , R_L , V_{CEsat} , what's the maximum current this source can provide. ($I_C \approx I_E$) * remember $V_{CE} \geq V_{CEsat}$ *

$$V_{CC} = V_{CE} + I_C R_L + I_E R_E \rightarrow V_{CE} = V_{CC} - I_C (R_L + R_E) \geq V_{CEsat}$$

then

$$I_C \leq \frac{V_{CC} - V_{CEsat}}{R_L + R_E}$$

Q2 Find R_E so a $I_C = 0.5A$ flows through the load, $V_B = 3.2V$

(assuming transistor action condition)

$$I_C = 0.5A \rightarrow I_C \approx I_E \rightarrow I_E = \frac{V_E}{R_E} = \frac{V_B - V_{drop}}{R_E}$$

$$R_E = \frac{V_B - V_{drop}}{I_E} = 5.2\Omega$$

Q3

What is the maximum value of the load resistor with $I_C = 0.5$, $V_E = 15V$

* or how big can you make R_L so it stays in linear active region *

$$V_{CC} = I_C R_L + I_E R_E + V_{CE} \rightarrow V_{CE} = V_{CC} - I_C R_L - I_E R_E \geq V_{CEsat}$$

$$R_L \leq \frac{V_{CC} - I_E R_E - V_{CEsat}}{I_C}, \begin{cases} R_E \text{ is fixed} \\ \text{above} \end{cases}, \begin{cases} \text{if past saturation} \\ I_C \approx I_E \end{cases} = 24.4\Omega$$

as R_L gets bigger it takes up a larger fraction of V_{CC} meaning V_{CE} gets lower pushing it into saturation

Q4 If $R_L = 10\Omega$ what value of V_B will put transistor into saturation?

as V_B gets bigger, I_B goes up causing a larger proportion to drop across R_E , which makes V_{CE}

in linear active region $V_{CE} > V_{CEsat}$

at saturation

$V_{CE} = V_{CEsat}$

$I_E \approx I_C$

actually looks at load

$$V_{CC} = I_C R_L + I_E R_E + V_{CE} \approx I_E (R_L + R_E) + V_{CE}$$

$$\Rightarrow I_E \approx \frac{V_{CC} - V_{CE}}{R_L + R_E}$$

$$V_B = V_{drop} + I_E R_E \approx \frac{V_{CC} - V_{CE}}{R_L + R_E} R_E + V_{drop}$$

plug in V_{CEsat}
you can rearrange
to solve for V_B


$$V_B \leq \frac{V_{CC} - V_{CEsat}}{R_L + R_E} R_E + V_{drop} \approx 5.7V$$

Amplifier

universal DC bias circuit

→ Devise a circuit that keeps the transistor operating in the linear active region

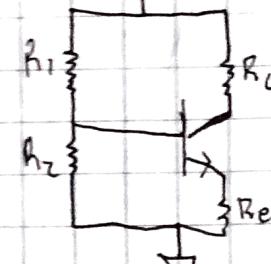→ Sets the constant DC operating conditions into AC to operate amplifier




Vcc & voltage source


- R_{b1} and R_{b2} form a voltage divider
- R_{b1} and R_{b2} complete the circuit
- other bias circuits can be derived from this one

From this thing you can make

(1)


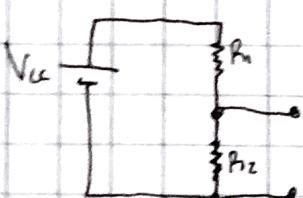


(2)

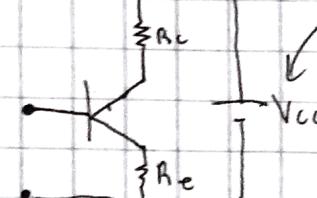

this is accurate b.c.

also V_{ce} is across both parts

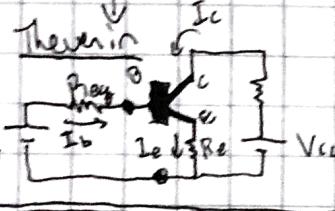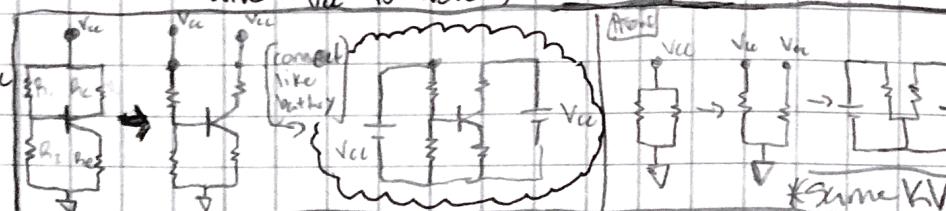

where:

$$V_{eb} = V_{cc} \left(\frac{R_1}{R_1 + R_2} \right), \quad I_{eb} = \frac{V_{cc}}{R_1 + R_2}$$

$$\text{KVL: } V_{cc} - I_b R_{b1} - V_{be} - I_e R_e = 0$$

[Voltage drop across diode] Voltage drop across diode

$$V_{cc} - I_c R_c - V_{ce} - I_e R_e = 0$$

Using these equations along with $I_e = I_c + I_b$, $I_L = \beta I_b$ to get $\frac{I_c}{I_b} \frac{I_b}{V_{cc}}$ operating point

$$1 \quad I_b = \frac{V_{cc} - V_{be}}{R_{b1} + (\beta + 1) R_e}$$

Plugging in
V_{cc}: known

$$I_b \left[\frac{R_1 R_2}{R_1 + R_2} + (\beta + 1) R_e \right] = \left(\frac{R_2}{R_1 + R_2} \right) V_{cc} - V_{be}$$


$$2 \quad V_{ce} = V_{cc} - I_c \left(R_c + \frac{\beta + 1}{\beta} R_e \right) \rightarrow \text{rearrange}$$

$$R_c + \left(\frac{\beta + 1}{\beta} \right) R_e = \frac{V_{cc} - V_{ce}}{I_c}$$

* Operating point is the DC voltage or current at a specific terminal of an active device with no input signal applied *

Side note: if input varies from 0-1V you could configure transistor to multiply by 5 so it goes from 0-5V. If you want to do 1000 but your supply is only 5 then it will only go between 0 and 4.5V.

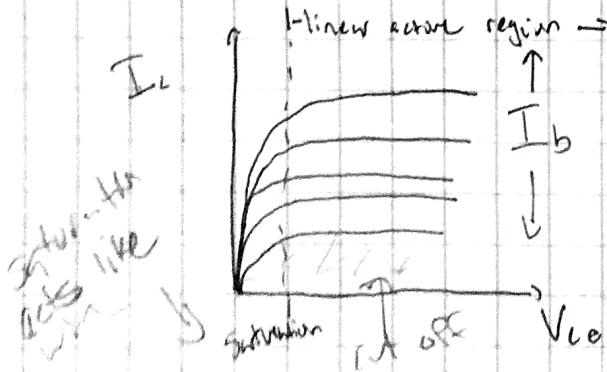The whole circuit keeps transistor in linear active region, its DC mode.



by connecting to a V_{cc} you can amplify, buffer or input stage

Biassing is the process of providing DC voltage which helps in the functioning of the circuit. A transistor is biased in order to make the emitter-base junction forward biased and the collector-base junction reverse biased, so it remains in linear active region (to work as an amplifier).

V_{cc} drives all to E, low base current

Tips tricks overview

6

(open circuit)

- If V_{in} or $V_B < (V_{BE} = V_{threshold})$ then there is no flow (cut off).
- $V_{CE} > V_{CEsat}$ to be in linear active regime
 ↳ commonly we: $V_{ce} = V_{CE} + V_{out}$, V_{out} is voltage across emitter
 ↳ you then can use $I_C = \beta I_B \rightarrow I_C \approx I_E$ as $I_E = \frac{\beta+1}{\beta} I_C$
 • β is big

- If $V_{CE} < V_{CEsat}$ (acts like wire) ($I_C = I_E$)
 ↳ you are in saturation V_{CEsat} is small so its like

~ impedance seen by V_B is $Z_B = \frac{V_B}{I_B}$
 ↳ it's in linear active

$$V_{CE} = 0$$

Ex: $V_{in} = V_B = 0$ then $I_B = 0$
 $\sum R_L$ which means $I_C = 0$

\bullet $V_B = 0$, $I_B = 0$ then $V_{CE} = V_{CC}$ (cut off)
 \bullet $V_B = \text{big}$, $I_B = \text{big}$ (only if R_B is chosen correctly)
 then $I_C = \beta I_B$
 and $V_{CE} = \text{small}$ (saturation)

Amplifiers

[npn emitter follower can't sink current] pnp follower can't source current

Intro

7


Cut off state: (OFF STATE)

- ① If $V_{BE} < .7V$ (P region isn't biased enough so no flow) (Max voltage ever)

$I_L = 3V$

I_B
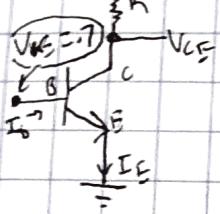
$$I_B \approx I_C = 0 \quad * \text{no voltage drop across } R \quad (V_{CE} = V_{CC} = 3V)$$



- ② $V_{BE} \approx .7V$ lets say $I_B = 10\mu A$, $\beta = 100$, $R_b = 1k\Omega$

$$I_C = \beta I_B = 1mA \quad \text{and} \quad I_{CR} = 1V$$

$$\rightarrow \text{so } 3V - 1V = V_{CE} = 2V \quad \text{AMPLIFIER}$$

Output across $V_{CE} = 2V$, 1 mA

Input = $10\mu A$, $\cancel{I_B}$ I think V_{BE} increasing so I_B increases

$$\rightarrow I_B = 30\mu A \rightarrow I_C = 3mA \quad \text{As } I_{CR} = 3V \quad \text{so } V_{CE} = 0$$

$0 < I_B < 30\mu A \rightarrow I_C = \beta I_B \text{ and } 0 < V_{CE} < 3V$

C LINEAR ACTIVE REGION

$I_B > 30\mu A \rightarrow I_C = 3mA \text{ (maximum) } V_{CE} = 0 \text{ min}$


Saturation State \uparrow (ON STATE)

*Saturation it's fully conducting \uparrow Cut off not conducting
 ↳ acts like wire \rightarrow \uparrow acts like open circuit

Transistor as a Voltage Amplifier

We want: $V_{out} = 10V_{in}$ but it's also important if $\Delta V_{out} = 10\Delta V_{in}$, which means a DC offset can amplify
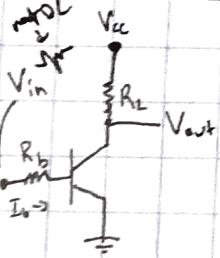
$$\Delta V_{out} = 10 \Delta V_{in} \quad * \text{assume in active state*} \quad I_C = \beta I_B$$



* V_{BE} is not DC current so I_C and I_B change in time $\rightarrow \Delta I_C = \beta \Delta I_B$

$$\rightarrow [V_{CC} - V_{out} = I_C R_L] \Delta \rightarrow, \text{ take } \Delta \text{ definition} \quad [-\Delta V_{out} = R_L \Delta I_C]$$

$$[V_{in} - V_{BE} = I_B R_b] \Delta \rightarrow \Delta V_{in} = \Delta I_B R_b$$

Then:

$$\frac{\Delta V_{out}}{\Delta V_{in}} = -\frac{R_L}{R_b} \frac{\Delta I_C}{\Delta I_B} = -\frac{R_L}{R_b} \beta$$

$$-\frac{R_L}{R_b} \beta \rightarrow \text{Voltage gain}$$

minus sign just flips magnitude
increase V_{in}

$I_B \uparrow$ then
 $I_C \uparrow$ (more drop across R_L) then $V_{out} \downarrow$

(ex)

