


Operational Amplifiers

- black box (complicated)

- plus and minus don't specify polarity on V_{in} (V_{in}^+ , V_{in}^-)

1

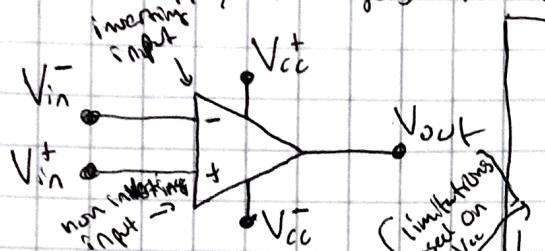- Power supply voltages (V_{cc}^+ and V_{cc}^-)




$$V_{out} = G(V_{in}^+ - V_{in}^-)$$

$$V_{sat}^- \leq V_{out} \leq V_{sat}^+$$

→ Output voltage can only be within a range set by 2 saturation voltages

[you might think huge output where $V_{sat}^+ \approx V_{cc}^+ - 1V$ (a little below pos power supply),
voltages (G is like 10^6) but
and $V_{sat}^- \approx V_{cc}^- + 1V$ (a little above the neg power supply)
points of V_{in}^+ and V_{in}^- have very high impedance so very little current flows into these points
output current is restricted | * takes a very small difference between V_{in}^+ and V_{in}^- to saturate]

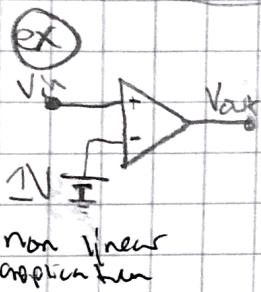Use 1 Comparator → compares V_{in}^- and V_{in}^+ and gives pos or neg depending on which is larger




* Here we have a random signal V_{in} and 1V battery
* When $V_{in} < 1$ it hits V_{sat}^- , (large gain quickly brings it there)
when $V_{in} > 1$ it hits V_{sat}^+

(Here is what) → Golden Rules
OpAmps are more generally used for

1. Output will make V_{in}^+ and V_{in}^- equal $\rightarrow \frac{V_{out}}{G} \approx 0 = V_{in}^+ - V_{in}^-$
2. No current flows into the inputs

Feedback Circuits

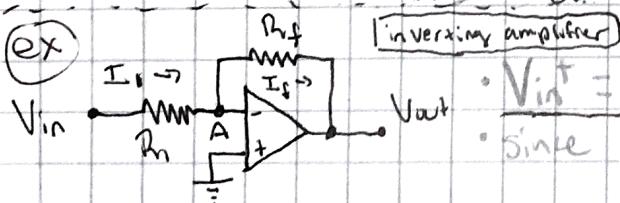

[inverting amplifier]

- $V_{in}^+ = 0$ so point A = 0 too
- Since A is "ground" too

$$V_{in} = I_i R_i ; A$$

$$\text{KVL at part A: } V_A - I_f R_f - V_{out} = 0 \text{ or } V_{out} = -I_f R_f \quad \text{Start at } V_{in} = A$$

$$V_{out} + I_f R_f = 0$$

Now use rule 2 that \rightarrow draw little current so $I_i = I_f$


then $V_{out} = -\frac{R_f}{R_i} V_{in}$ (- signal inverted)

* Input resistance is just the effective resistance between the input terminals.

↳ input terminals here are V_{in} and ground, since A is ground too $\rightarrow R_{in} = R_i$

Non-inverting amplifier

Using rules

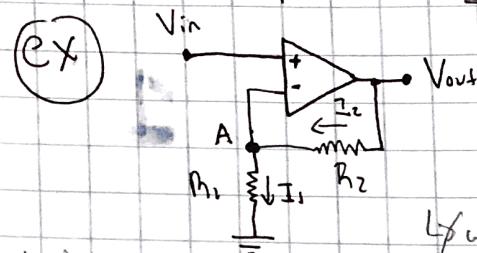

$$V_{in} = V_A \text{ and } I_2 = I_1$$

2

$$\text{loop (-) input to ground: } V_A = I_1 R_1$$

$$\text{loop Vout to ground: } V_{out} = I_2 R_2 + I_1 R_1$$

(we know)
 $V_A = V_{in}$

$$\text{and } V_A = I_1 R_1 = I_2 R_2$$


$$U_{in, ref} \quad I_1 = I_2$$

$$\rightarrow V_{out} = I_1 R_2 + V_{in} = V_{in} \frac{R_2}{R_1} + V_{in} = V_{in} \left(1 + \frac{R_2}{R_1} \right) = V_{out}$$

idk why ??

* input impedance $= \infty$

(ex)

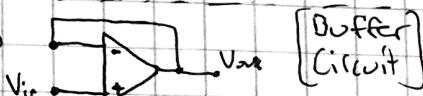


$$V_{out} = V_{in} \text{ and by rules}$$

$$V_{in}^+ = V_{in} \text{ so } V_{out} = V_{in}$$

Used between a high impedance voltage source and a low impedance load to alleviate loading

(ex) Adder Circuit

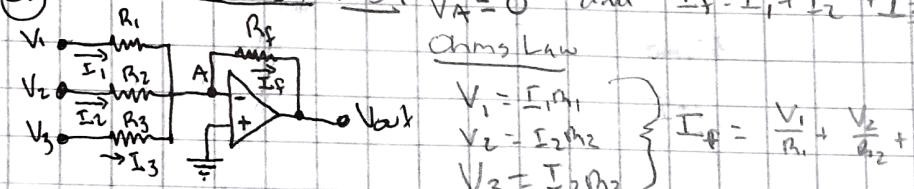

* $V_A = 0$ and $I_f = I_1 + I_2 + I_3$

Ohm's Law

$$\begin{aligned} V_1 &= I_1 R_1 \\ V_2 &= I_2 R_2 \\ V_3 &= I_3 R_3 \end{aligned} \quad \left\{ \begin{aligned} I_f &= \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \end{aligned} \right.$$


$$V_{out} = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

\rightarrow we got a weighted sum based on resistors

\rightarrow if we wanted to add normally we make $R_1 = R_2 = R_3 = R_f$

(can easily extend to N.A.)

(ex) Subtract circuit (differential)

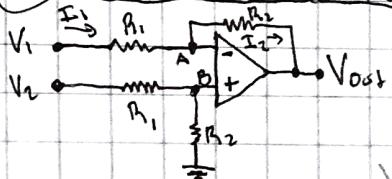

$$* V_A = V_B \text{ and } I_1 = I_2 \times$$

① check bottom

$$V_2 - I_1 R_1 - I_2 R_2 = 0$$

$$V_B = I_2 R_2$$

KVL: $V_A - I_1 R_1 - V_A = 0 \rightarrow I_1 = \frac{V_A - V_B}{R_1}$

$$V_A - I_1 R_1 - V_A = 0 \rightarrow I_1 = \frac{V_A - V_B}{R_1}$$


$$\therefore V_{out} + I_2 R_2 - V_A = 0$$

$$\frac{R_2}{R_1} (V_B - V_A) = V_{out}$$

[putting these 3 together]

$$V_{out} = V_A - I_2 R_2 = \frac{R_2}{R_1 + R_2} V_2 - \left(\frac{V_1}{R_1} + \frac{R_2}{R_1 + R_2} \frac{V_1}{R_1} \right) R_2 =$$

Integrator

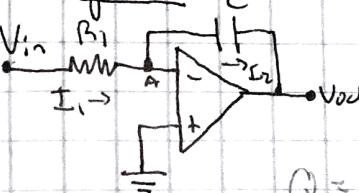

$$* V_A = 0 \quad I_1 = I_2 \times$$

$$V_{in} = I_1 R_1$$


$$\text{KVL } V_{out} - \frac{Q}{C} - V_A = 0$$

$$Q = \int I_2 dt = \int I_1 dt$$

$$V_{out} = - \frac{Q}{C} = - \frac{1}{C} \int I_1 dt =$$

$$V_{out} = - \frac{1}{R_1 C} \int V_{in} dt$$

Differentiator

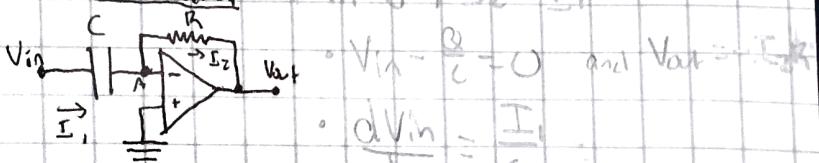

$$* V_A = 0 \quad I_2 = I_1 \times$$

$$V_{in} - \frac{Q}{C} = 0 \quad \text{and } V_{out} = I_1 R_1$$

$$\frac{dV_{in}}{dt} = \frac{I_1}{C}$$


$$V_{out} = - R_1 C \frac{dV_{in}}{dt}$$

(or integral & output sum law applies)
per integrator far depends what var

Operational Amplifiers Part 2

3

High Pass

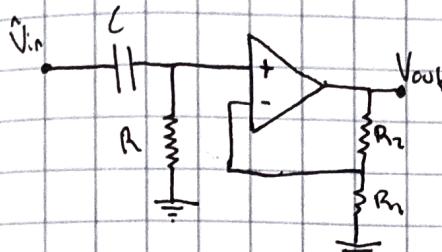

Golden Rules: $V_+ = V_-$ and little current into $\overset{+}{\text{I}}$

$$\begin{aligned} \text{KVL: } & \textcircled{1} \quad \hat{V}_{in} - iZ_C - iR_h = 0 \rightarrow \hat{V}_{in} - i(Z_C + R_h) = 0 \\ & \textcircled{2} \quad \hat{V}_{in} - iZ_C - V^+ = 0 \rightarrow i = \frac{\hat{V}_{in} - V^+}{Z_C} \end{aligned}$$

$$\begin{aligned} & \textcircled{3} \quad \hat{V}_{out} - i_2 R_2 - i_1 R_1 = 0 \rightarrow \hat{V}_{out} = i_2 (R_1 + R_2) \\ & \textcircled{4} \quad V^- - i_2 R_1 = 0 \rightarrow i_2 = \frac{V^-}{R_1} \end{aligned}$$

$$\textcircled{5} \quad \hat{V}^- = \hat{V}_{out} \frac{R_1}{R_1 + R_2}$$

$$\textcircled{6} \quad \hat{V}_{in} = \frac{\hat{V}_{in} - V^+}{Z_C} (Z_C + R_h) \rightarrow \hat{V}_{in} - \hat{V}_{in} \frac{Z_C}{Z_C + R_h} = V^+ \Rightarrow V^+ = \hat{V}_{in} \left(1 - \frac{Z_C}{Z_C + R_h}\right)$$


$$\hookrightarrow \hat{V}^+ = \hat{V}_{in} \frac{R_h}{Z_C + R_h} = \hat{V}_{in} \frac{R_h}{R_h + \frac{1}{\omega C}} \quad \text{simplyfying}$$

$$\text{Combine } (V_+ = V_-): \quad \hat{V}_{out} \frac{R_1}{R_1 + R_2} = \hat{V}_{in} \frac{R_h}{R_h + \frac{1}{\omega C}} = \hat{V}_{in} \frac{R_h \omega C (R_h \omega C + j)}{(R_h \omega C)^2 + 1}$$

$$\hookrightarrow \boxed{\hat{V}_{out} = \hat{V}_{in} \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_h \omega C^2 + j R_h \omega C}{(R_h \omega C)^2 + 1} \right)} \quad \text{when } \omega \rightarrow \infty: \hat{V}_{out} = \hat{V}_{in} \frac{R_1 + R_2}{R_1}$$

Low Pass

Seeing how above its voltage divider!

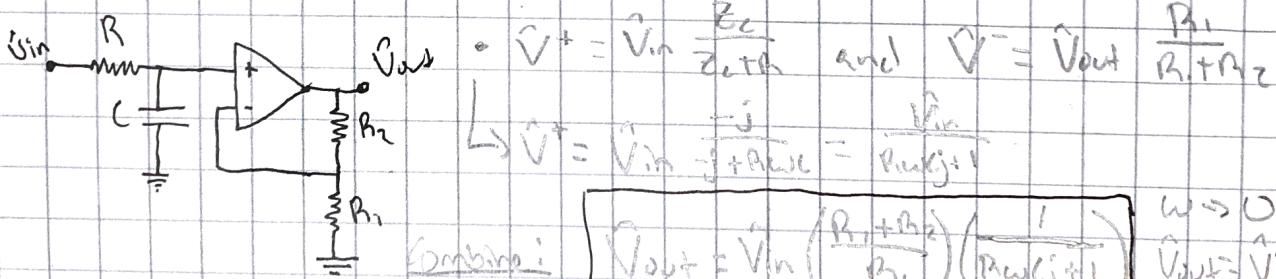


$$\hat{V}^+ = \hat{V}_{in} \frac{Z_C}{Z_C + R_h} \quad \text{and} \quad \hat{V}^- = \hat{V}_{out} \frac{R_1}{R_1 + R_2}$$

$$\text{Combining:} \quad \boxed{\hat{V}_{out} = \hat{V}_{in} \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{1}{R_h \omega C j + 1} \right)}$$


$$\text{when } \omega \rightarrow 0: \quad \hat{V}_{out} = \hat{V}_{in} \frac{R_1 + R_2}{R_1}$$

you can invert a low pass

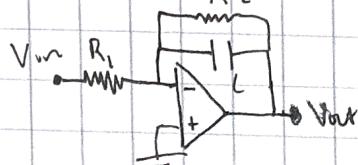

$$\hat{V}_{out} = -\hat{V}_{in} \frac{R_2}{R_1} \frac{1}{R_h \omega C j + 1}$$

you can invert a high pass

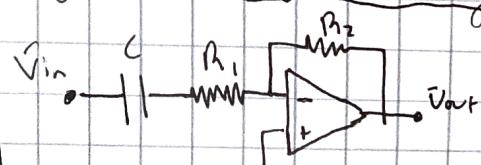

$$\hat{V}_{out} = -\hat{V}_{in} \frac{R_2 \omega C}{R_1 \omega C - j}$$


Practical Considerations for the Operational Amplifier

4

- Actually a small amount of current does flow into the op-amp
- ↳ I_B^+ and I_B^- ($\sim 500 \text{ nA}$) but under certain conditions they can cause large effects
- (Ex) normal non-inverting amplifier, but w/ a capacitor
 - could be trying to filter out DC signal BUT
 - output will be saturated at V_{sat} and unresponsive to input
 - blocked dc current and OP won't work what if ????

What if we have:

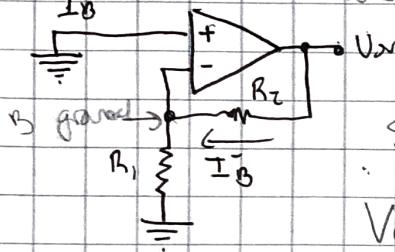non-inverting amplifier but the output is grounded



* could be testing the circuit


↳ if input = 0 we expect output = 0

Since point B is ground no current through R_f ,

but $I_B^+ = I_B^-$ & avoid large feedback resistors

$$V_{out} = I_B^- R_f = 0.5 \text{ V}$$

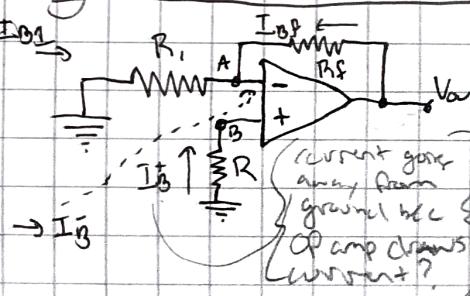You can minimize bias current (Buffer Circuit)



grounded inputs since we are interested in bias effects

$$\text{KVL } V_B^+ + I_B^+ R_f = 0 \rightarrow V_B^+ = -I_B^+ R_f \quad (\text{By rule } 1 = A)$$

$$\text{KCL } I_B^- = I_{Bf} + I_{B1}$$

$$V_A^- + I_{B1} R_f = 0 \rightarrow I_{B1} = -\frac{V_A^-}{R_f}$$

$$V_{out} - I_{Bf} - V_A^- = 0 \quad I_{Bf} = \frac{V_{out} - V_A^-}{R_f}$$

$$I_B^- = -\frac{V_A^-}{R_f} + \frac{V_{out} - V_A^-}{R_f}, \quad V_A^- = V_B^+, \quad I_B^- = I_B^+ \frac{R_f}{R_f + R_B} + I_B^+ \frac{R_f}{R_f + R_B}$$

$$\hookrightarrow V_{out} = I_B^- R_f - I_B^+ R_f \left(1 + \frac{R_f}{R_B}\right) \quad \text{and if you choose a resistor such}$$

$$\text{that } R_f = \frac{R_B R_f}{R_B + R_f}, \quad V_{out} = R_f (I_B^- - I_B^+) \quad \text{which is difference of currents}$$

[for real op amps max difference
is specified as the input offset voltage]

$$\rightarrow I_{os} = I_B^- - I_B^+, \quad I_{os} \leq I_B^+ / 4$$

Some high
quality op-amps
can do
 $I_B^- \leq 0.05 \text{ nA}$


Slew Rate in the OP Amp

5

↑ Slew is good

- Suppose we suddenly change the input for our OP amp

How fast will the output change?

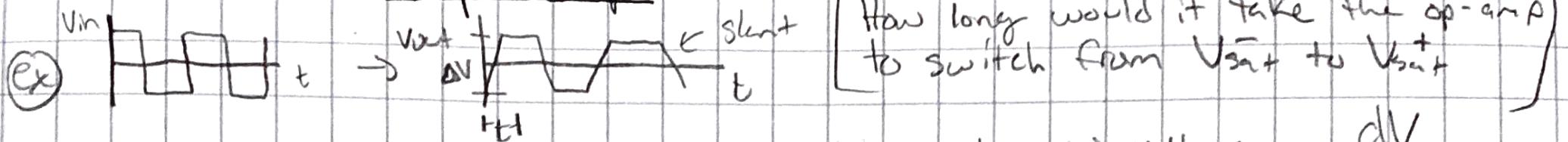

$$\hookrightarrow V_{cc}, V_{ee} = \pm 15V, V_{sat}^+ = \pm 14V \rightarrow \text{Slew rate} =$$

$$\hookrightarrow \text{Slew rate}, t = \frac{\Delta V}{\text{slew}} = \frac{28V}{15V/\mu s} = 56\mu s$$

$$\frac{\text{change in voltage}}{\text{change in time}} = \frac{dV}{dt}$$

Time time

Ex) Imagine you have $\text{Output} = A \sin(\omega t) \rightarrow \frac{dV}{dt} = \omega A \cos(\omega t)$

\hookrightarrow To avoid slew rate limiting we want max rate of change < slew rate

You don't want the waveform changing faster than the slew rate

$$\hookrightarrow \omega A < \text{slew} \rightarrow f_{max} = \frac{\text{slew}}{2\pi A} \approx 8 \text{ kHz}$$

Above a certain frequency the output "charge up the load" can't follow the signal


↑
decreasing
amplitude makes
it better

\rightarrow When $A = V_{sat}$ is called "full power bandwidth"

6

Astable multivibrator

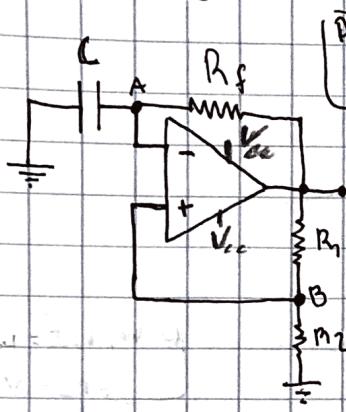initially $V_A = V_B = V_{out} = 0$ (not stable)



Phase
1

w/ some noise $V_B > V_A$: w/ $V_{out} = G(V_B - V_A)$

V_{out} gets pushed to V_{sat}^+ so $V_{out} = V_{sat}^+$

$$\rightarrow V_B = V_{out} \frac{R_2}{R_1 + R_2} = V_{sat}^+ \frac{R_2}{R_1 + R_2} \quad (V_{out} = G(R_1 + R_2)) \quad (V_{sat} = 5R_2)$$

this happens instantly...

now the capacitor will start to charge! (slowly)

Since $V_{out} > V_A$ and V_A is hooked up to ground a current starts!

$$V_A = \frac{Q}{C} \quad (\text{Voltage across capacitor by KV})$$

initial charge

$$Q(t) = V_A(0) + \frac{1}{C} \int I dt$$

charging

[general equation for voltage on capacitor] $\rightarrow V_A(t) = V_A(0) + \frac{1}{C} \int \frac{V_{out} - V_A}{R_f} dt$ ①

to find the current \rightarrow $V_{out} - IR_f - V_A = 0 \rightarrow V_A(t) = V_A(0) + \frac{1}{C} \int \frac{V_{out} - V_A}{R_f} dt$

Phase
2

now capacitor is charging b/c $V_A(t)$

+ goes to V_{sat} !!

now $V_B = V_{out} \frac{R_2}{R_1 + R_2} = V_{sat}^+ \frac{R_2}{R_1 + R_2}$ now the capacitor is discharging

!! key when it's initial & final!! $\rightarrow V_A(t) = V_A(0) + \frac{1}{C} \int \frac{V_{out} - V_A}{R_f} dt = V_{sat}^+ \frac{R_2}{R_1 + R_2} + \frac{1}{C} \int \frac{V_{sat}^+ - V_A}{R_f} dt = V_A(t)$ ②

discharging

• till keep going when $V_A(t) \leq V_B = V_{sat}^+ \frac{R_2}{R_1 + R_2}$, $V_{out} = V_{sat}^+$, slowly charging... $V_B = V_{sat}^+ \frac{R_2}{R_1 + R_2}$

$$\rightarrow V_A(t) = V_{sat}^+ \frac{R_2}{R_1 + R_2} + \frac{1}{C} \int \frac{V_{sat}^+ - V_A}{R_f} dt$$

General switches at V_S when $V_A = V_S$

general eq for a capacitor discharging

$$V_A = V_1 e^{-\frac{t}{R_f C}} + V_2$$

and our limits

* never actually reached it switches

($t=0 \rightarrow V_A = -V_1$) and ($t \rightarrow \infty, V_A \rightarrow V_{sat}^+$)

$$① V_2 = V_{sat}^+ \rightarrow \text{and } ② -V_1 = -V_{sat}^+ \frac{R_2}{R_1 + R_2} = V_1 + (V_2 - V_{sat}^+)$$

$$\rightarrow V_1 = -V_{sat}^+ \left[\frac{R_2}{R_1 + R_2} + 1 \right]$$

then plugging all in

$$V_A = -V_{sat}^+ \left[\frac{R_2}{R_1 + R_2} + 1 \right] e^{-\frac{t}{R_f C}} + V_{sat}^+$$

the time t_0 when $V_A = (+V_S = V_{sat}^+ \frac{R_2}{R_1 + R_2})$

$$t_0 = R_f C \ln \left(1 + \frac{2 R_2}{R_1} \right)$$

* no V_{sat}^+ controls out voltage as in power no effect

$$V_S = \pm V_{sat}^+ \frac{R_2}{R_1 + R_2}$$

Chap 7 2, 3, 5

[from general charging capacitor eq]

The other of amp is at $\frac{2}{3}V_{cc}$ so when it hits this Vout switches and discharges

$$(2) \text{ charges } V_{2,6} = \frac{-2V_{cc}}{3} e^{-\frac{t}{(R_1+R_2)C}} + V_{cc} \text{ (from } \frac{V_{cc}}{3} \text{ to } \frac{2}{3}V_{cc})$$

$$\hookrightarrow \frac{2}{3} = \frac{-2}{3} e^{-\frac{t}{R_1+R_2}} + 1 \rightarrow \frac{1}{2} = e^{-\frac{t}{R_1+R_2}} \rightarrow -(R_1+R_2)(\ln(\frac{1}{2})) = t_{on}$$


$$(3) \text{ turn on for } 4 \text{ hrs} = 14400 \text{ sec} = (R_1+R_2)(\ln(2))$$

$$R = R_1 = R_2 \rightarrow$$

$$10387.404 = RC$$

$$\left\{ \begin{array}{l} C = 1 \text{ Farad (can buy on amazon)} \\ R = 10.387 \text{ k}\Omega \end{array} \right.$$

$$V_{out} = 6(V_+ - V_-)$$

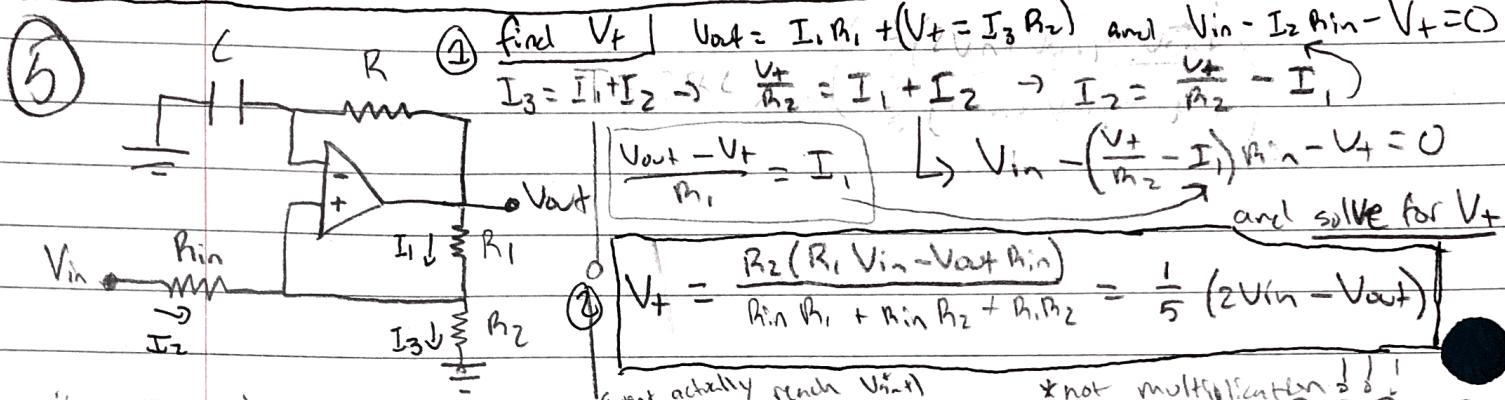

(3) $V_- = V_1 e^{-\frac{t}{R_1 C}}$ initial $\{t=0, V_- \rightarrow V_{sat}\}$ $\{V_+ \rightarrow V_{sat}\}$

$V_+ = V_1 e^{+\frac{t}{R_1 C}}$ final $\{t=\infty, V_+ \rightarrow V_{sat}\}$ $\{V_- \rightarrow V_{sat}\}$

(5) Right: when charging starts ($-V_S$) the capacitor just reached (V_{sat})
 ↳ "done" happens when $V_+ < V_-$ but while it's discharging $V_+ < V_- \rightarrow (V_{out} \rightarrow V_{sat})$
 to → (when it hits this it discharges)

$$V_2 = V_{sat}$$

$$V_+ [V_{out} = V_{sat}] - V_{sat} = V_1$$

$$V_+ = (V_1 [V_{out} = V_{sat}] - V_{sat}) e^{-\frac{t}{R_1 C}} + V_{sat}$$


$$V_{out} = 6(V_+ - V_-)$$

$$V_- = V_+ [V_{out} = V_{sat}] = +V_S$$

fat its "done" point
 $V_+ < V_-$ (flips to V_{sat})


$$V_+ [V_{out} = V_{sat}] = (V_1 [V_{out} = V_{sat}] - V_{sat}) e^{-\frac{t}{R_1 C}} + V_{sat}$$

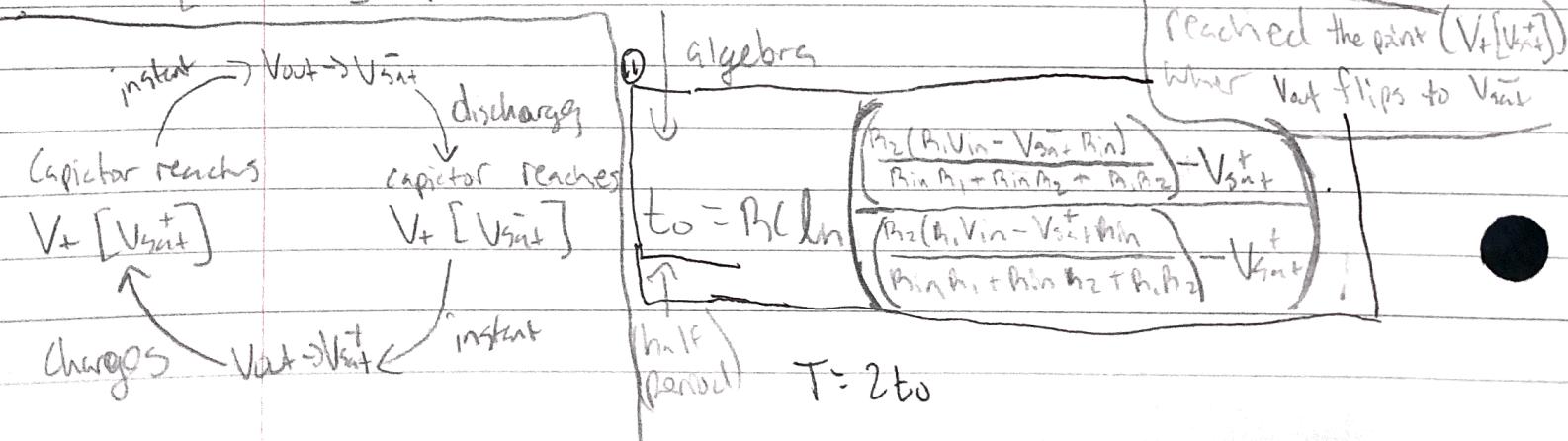But the capacitor just reached the point ($V_+ [V_{sat}]$)





555 timer
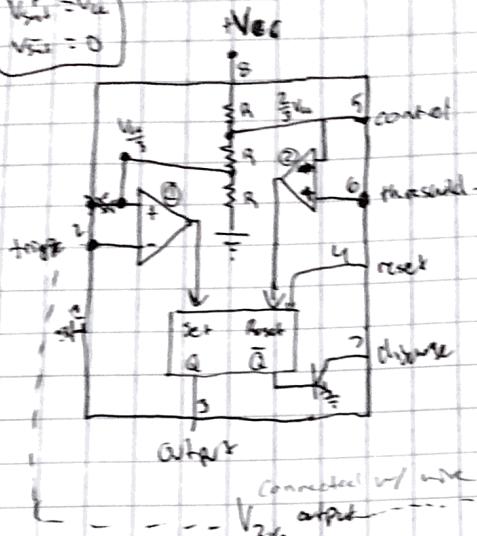
$$\begin{cases} V_{out} = V_{cc} \\ V_{out} = 0 \end{cases}$$



Register / compare configuration to generate oscillation

→

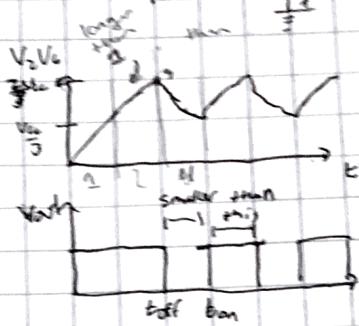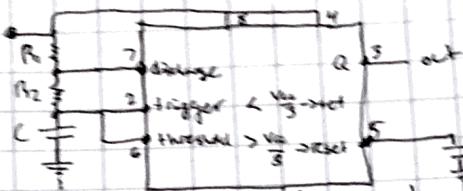

Input	State	Q	\bar{Q}
0	Reset	0	1
1	Set	1	0
0	Reset	0	1
1	Stay	1	0
0	Stay	0	1
1	Reset	0	1

- $V_{at} = 6(V_+ - V_-) \rightarrow$ Op amp ① $V_{at} \rightarrow \text{Set}$
 $V_+ \rightarrow \frac{V_{cc}}{3}$
 $(V_2 = V_-) \rightarrow \text{trigger}$
- big figure is inside w/
Op amps.

small figure is oscillator

as soon as one side is bigger than other it goes to that circuit

- Op amp ② $V_{at} \rightarrow \text{Reset}$
 $V_+ \rightarrow \frac{2}{3}V_{cc}$
 $(V_2 = V_-) \rightarrow \text{threshold}$

1 Capistor is uncharged. $0 < V_{2,0} < \frac{1}{3}V_{cc}$

Op amp ① $V_{at} = 6(V_+ - V_-) \rightarrow V_- = 0$ and $V_+ = \frac{V_{cc}}{3} \rightarrow V_{at} = V_{2,0}$

Set = 1 $V_2 = 0$ but the high V_{at} sets the flip flop

Op amp ② $V_{at} = 6(V_+ - V_-) \rightarrow V_+ = 0$, $V_- = \frac{2}{3}V_{cc} \rightarrow V_{at} = 0$ Starts to charge!

Reset = 0 $V_2 = 0$ and $V_{at} < 0$ has no reset might be V_{at} when $V_{2,0}$ reaches 0.

The op-amps voltage is the capacitor $V_{2,0}$ *

2 lets say Opamp ① stays & pass $\frac{V_{cc}}{3}$ (not $\frac{2}{3}V_{cc}$) "Stay"

Set = 0 $V_- \rightarrow V_+ \rightarrow V_{2,0} = 0$

Then Opamp ② is still 0 $V_+ < V_- \rightarrow V_{2,0} = 0$

3 Capistor charges pass $\frac{2}{3}V_{cc}$ (Opamp 2 still Set = 0, $V_- \rightarrow V_+$ $\rightarrow V_{2,0} = 0$)

Set = 0

Opamp ② $V_+ > V_- \rightarrow V_{at} = V_{2,0}$

Reset = 1

Capistor now discharges through the transistor

→ [discharges through stay phase] or
 until set turns to 1 again

• charge $V_{2,6} = -\frac{2V_{cc}}{3} e^{i \frac{t}{(R_1 + R_2)C}} + V_{cc}$ (from $\frac{V_{cc}}{3}$ to $\frac{2V_{cc}}{3}$)

• discharge $V_{2,6} = \frac{2}{3} V_{cc} e^{-\frac{t}{R_2 C}}$ (from $\frac{2V_{cc}}{3}$ to $\frac{V_{cc}}{3}$)

$$t_{on} = (R_1 + R_2) C \ln(2)$$

$$t_{off} = R_2 C \ln(2)$$