

Chapter 25 notes

- Charges in motion \rightarrow current
- electric circuits convey energy from one place to another
- charged particle move, electric potential is transferred from a source to a device where energy is stored, converted to another form
~ sound, heat, light

- Before $\vec{E} = 0$ in a conductor so no net current, charges do move randomly, just add to
- put \vec{E} field inside a conductor

\rightarrow particles experience a force $\vec{F} = q\vec{E}$ {in a vacuum it would accelerate}
but its in a conductor, frequently collides with massive stationary ions.
 \vec{F}_{net} is an addition to the random motion inside so it doesn't cancel but moves!

The particles slowly move with velocity $\vec{v}_{drift} \rightarrow$ NOW A current!

$v_{particle} = 10^6 \text{ m/s}$

$v_{drift} = 10^{-4} \text{ m/s}$



without E_{field}
with E_{field}
net displacement
($v_d \Delta t$)



The reason your light turns on instantly?

\rightarrow E_{field} is activated near speed of light
 \rightarrow which moves all the electrons at once.

So it would take awhile for an electron to move far, they just all move together, called by the E_{field}

* E_{field} does work, causing them to move & bump, heating up wires

in germanium in silicon, "positive charges can move", really just the absence of e^- that move called "holes".




$I =$ flow of charge whether or not the charges are free it can just be those "holes"

$I = \frac{dq}{dt}$

ampere = $\frac{1C}{s}$

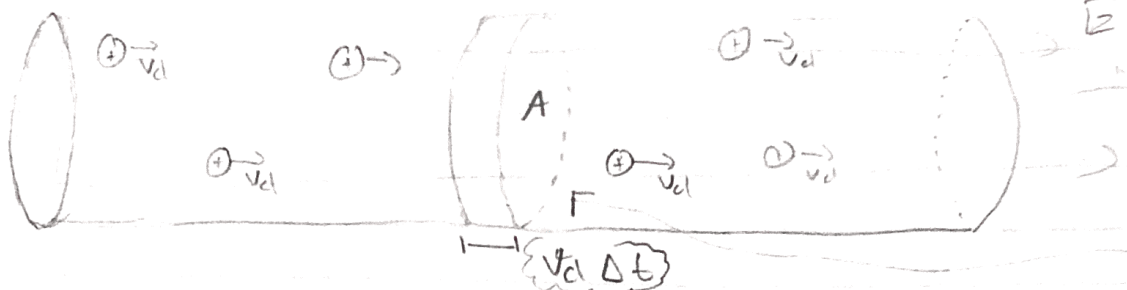current is the net charge moving through a cross sectional Area per unit time



- there are " n " moving particles per unit volume = concentration
- all move same " v_d " in a time interval dt
- so they make a distance $v_d dt$
- Volume of this cylinder is $A \cdot v_d dt$

→ so n ($\frac{\# \text{ of particles}}{\text{volume}}$) so $n \cdot \text{Volume} = \# \text{ particles}$

→ $n \cdot A v_d dt$ ← q times this is the charge through this cylinder

→ $dQ = q [n \cdot A v_d dt]$

$$I = \frac{dQ}{dt} = nq v_d A$$

* units are $\frac{\text{Amp}}{\text{m}^2}$ → and current per cross-sectional area is $J = \frac{I}{A} = nq v_d$

* if $q = +$ the $v_d =$ to the right, if $q = -$, $v_d =$ to the left so signs cancel

Use |8|

or $\vec{J} = nq \vec{v_d}$

← I is just flow through a wire

\vec{J} is a vector because it tells us how charge flows at a certain point

\vec{J} normally depends on \vec{E} and properties of the material which can make it complex
 → but for some metals at given temps $\vec{J} \propto \vec{E}$, and $\frac{|\vec{E}|}{|\vec{J}|} = \text{constant}$

if this ideal picture is kept we have Ohm's law

resistivity $\rho = \frac{|\vec{E}|}{|\vec{J}|} \left[\frac{\text{V} \cdot \text{m}}{\text{A}} \right]$ or $(\Omega \cdot \text{meter})$ * $\frac{1}{\rho} = \text{conductivity}$

resistivity goes up when temp goes up (cause those ions shake more, hitting more e^-)
 $\rho(T) = \rho_0 [1 + \alpha(T - T_0)]$ $\alpha = \text{coefficient of resistivity}$ $\rho_0 = \text{resistivity at } T_0$

→ from this $\vec{E} = \rho \vec{J}$ to get to ohms law
 and explain this go to next paper!


$$J = \sigma E$$

~~σ~~

$$E = \frac{V}{L}$$

σ is conductivity

does that voltage pump work?

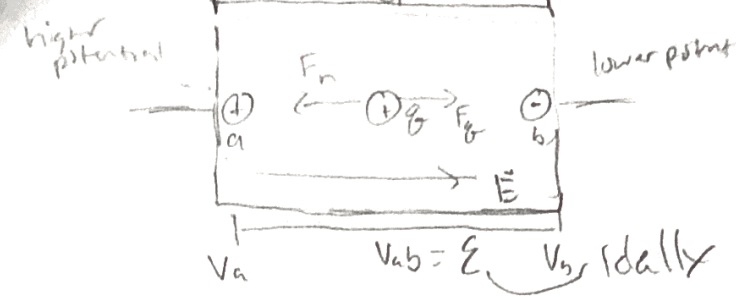

$$F_e = qE$$


F_n = counteracting force

pushes charges uphill

- if F_n wasn't there charge would flow until potential = 0

Origin of F_n depends on the source, a generator it uses magnetic field forces, in a battery \rightarrow diffusion process and varying electrolyte concentrations from chemical reactions, Van de Graaff uses mechanical, moving belt or wheel.

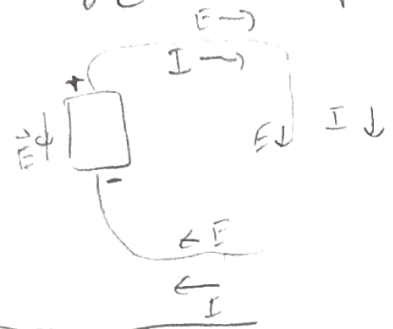$W_n = q\mathcal{E}$ so potential energy to move it ^{against F_e} is qV_{ab}



\mathcal{E} = constant potential difference

ideally $V_{ab} = \mathcal{E}$

the source has an internal resistance "r"

actually $V_{ab} = \mathcal{E} - Ir$

then $V_{ab} = IR$ so $IR = \mathcal{E} - Ir$ then $I = \frac{\mathcal{E}}{R + r}$

so $I = \frac{\mathcal{E}}{\text{total resistance through the circuit and source}}$

terminal voltage

think of it like $V_{directed}$ or V_{actual}


magnetic field units 1 T

Chapter 27, Magnets

- Fundamental nature of magnets is in the interaction of moving charges
- 1. moving charges produces a magnetic field 2. a second current responds and experiences mag. f
- a) a moving charge or current creates a magnetic field
- b) the mag field exerts a force on any other moving charge or current

\vec{B} = magnetic field

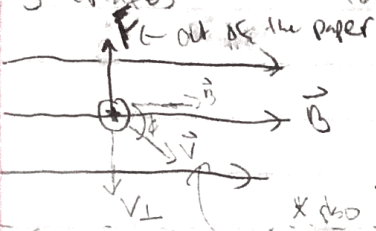\vec{B} creates a force but is always \perp




$$F = |q| v_{\perp} B = |q| v B \sin \phi$$

not deduced theoretically observation


$$\vec{F} = q \vec{v} \times \vec{B}$$

* if $90^\circ = F_{max}$ $\vec{F} = |q| v B_{\perp}$ $\cos B \sin \phi = B_{\perp}$

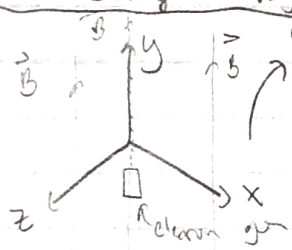* if using right hand rule on negative charges, \vec{F} is opposite from RHR



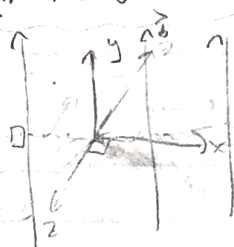if \vec{v} is \parallel to \vec{B} so $\phi = 0$ or π



if the is turned 90° $\phi = \frac{\pi}{2}$
 \vec{F} is going along z-dir


if a charged particle is in with a \vec{E} and \vec{B} the Force is $\vec{F} = q(\vec{E} + \vec{v} \times \vec{B})$

Magnetic Flux!

divide any surface into small dA 's for each element B_{\perp}

$$d\Phi_B = B_{\perp} dA = B \cos \phi dA = \vec{B} \cdot d\vec{A}$$

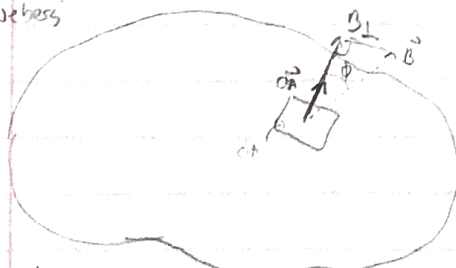SI units: Webers
 1 Wb
 $\frac{\text{N} \cdot \text{m}}{\text{A}}$




$$\Phi_B = \int B \cos \phi dA = \int B_{\perp} dA = \int \vec{B} \cdot d\vec{A}$$

if \vec{B} is uniform through a surface, $\Phi_B = B_{\perp} A = BA \cos \phi$

* Since there's no such thing as a monopole, so it's always a dipole the flux through a closed surface is zero. \leftarrow all field lines that exit, re-enter.

$$\oint \vec{B} \cdot d\vec{A} = 0$$

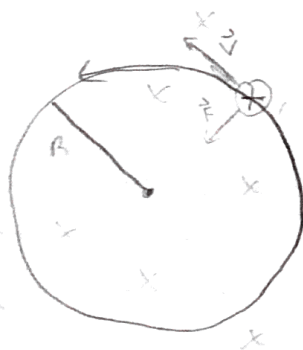if dA is at right angles to the field lines then $B_{\perp} = B$, $B = \frac{d\Phi_B}{dA}$



\vec{B} field comes out
neg. the CW
upper


$$R = \frac{mv}{|q|B}$$

$$F = |q|vB = \frac{mv^2}{R}$$

$$V = R\omega \rightarrow \omega = \frac{|q|B}{m} \rightarrow f = \frac{\omega}{2\pi}$$

f is lot of Hz, this is called cyclotron f , particles moving in circ paths are given a boost twice each revolution increasing energy and R but not ω or f

Velocity selectors

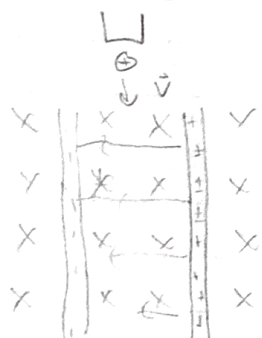

$$qE = qvB$$

F_B is to the left

F_E is to the right

particles


$$v = \frac{E}{B}$$

with speed

pass with no deflections

since forces cancel out

wires

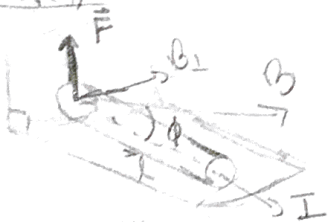

$$\vec{F} = q\vec{v}_d \times \vec{B} \text{ since } \vec{v}_d \text{ and } \vec{B}_\perp \text{ are } \perp \rightarrow F = qv_d B_\perp$$

n = number of charges per unit volume

total number of charges = nAl

$$F = (nAl)(qv_d B_\perp) = (nqv_d A)(lB_\perp) = I l B_\perp = I l B \sin \phi$$

force on all the moving chgs

$$\text{so } F = I l B \sin \phi = I \vec{l} \times \vec{B} \text{ and } d\vec{F} = I d\vec{l} \times \vec{B}$$

we can integrate to find total force on a conductor of any shape

this force causes wire to vibrate making sound


the magnet exerts a force on voice coil \propto the current in the coil

(oscillates from signal)

pg 600

Chap 27 notes cont...

Torque / magnetic fields

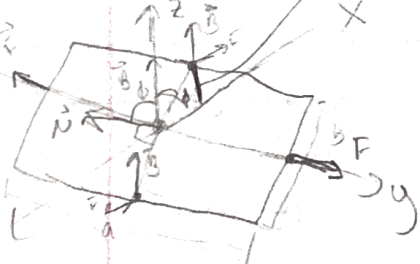

from $F = I \ell B \sin \phi$ side a $\Rightarrow F = I a B$
 and for b $\Rightarrow F = I b B \sin(90^\circ - \phi) = I b B \cos \phi$
 (since it turns 90°)

ϕ = angle between \vec{n} and \vec{B}

* net force = 0 but net torque $\neq 0$ usually $\tau = 0$ if $\phi = 0^\circ$

- the moment arm is the \perp distance from the rotational axis to the force, * Also just draw a line from F to rotational axis, then find \perp per

Thus:

$$\tau = 2 F \left(\frac{b}{2}\right) \sin \phi = I B \underbrace{ab}_{\text{area of loop}} \sin \phi = I B A \sin \phi$$

\uparrow angle between \vec{n} and field direction

* IA is called the magnetic dipole moment $\Rightarrow \mu = IA \Rightarrow \tau = \mu B \sin \phi$

$$\tau = \vec{\mu} \times \vec{B}$$


Potential Energy

$$U = -\vec{\mu} \cdot \vec{B} = -\mu B \cos \phi$$

number of turns \leftarrow each loop produces a torque



$$\tau = N \cdot IA \cdot B \sin \phi$$

(pg. 902)

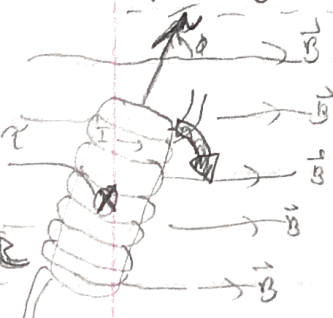

Direct current motor

→ rotational axis

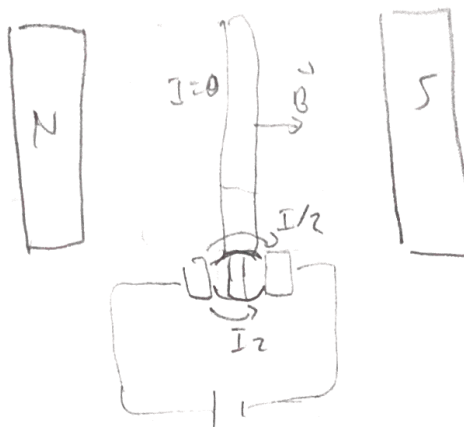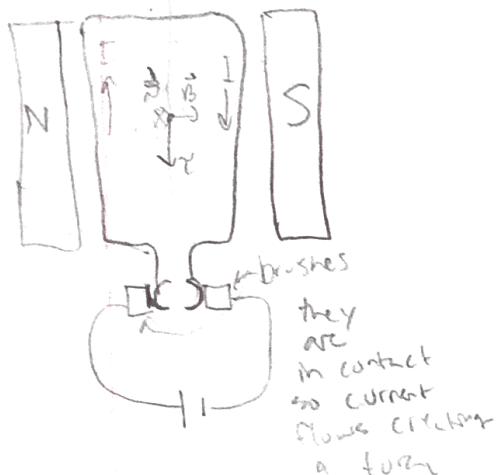

this time brushes are in contact with the open part so current just goes around the small loop

Power for electric motors:

Potential difference between the terminals = V_{ab}

$$I \cdot V_{ab} = \text{Power}$$

\mathcal{E} comes from magnetic forces exerted on currents in conductors of the rotor. The associated electromotive force is \mathcal{E} and called an induced emf or back emf because it is opposite to current.

$$V_{ab} = \mathcal{E} + I r_{\text{internal resistance}}$$

← series motor and rotor is in series with the machine

$$V_{ab} > \mathcal{E}$$

because the magnetic force is \propto to velocity \mathcal{E} is not constant but is \propto to the speed of rotation of the rotor

Hall effect 908.


$$\omega = 2\pi f$$

LC circuit

• shows oscillating current and charge

$$Q_m = C V_m \text{ capacitor eq.}$$

Wrench

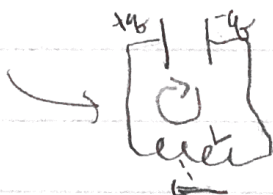

• capacitor begins to discharge

• causes emf in inductor (i can't change instantly)

• at each instant $V_m \Rightarrow \text{emf}$

• when $V_m = 0$ (emf = 0 too) I_m becomes maximal

now all energy is in inductor \vec{B} , The current persists though

• capacitor begins to charge again (flipped polarity though)

then repeats, starts cycle over

+ divide by $-L$ and $i = \frac{dq}{dt}$

$$-L \frac{di}{dt} - \frac{q}{C} = 0 \rightarrow \frac{d^2 q}{dt^2} + \frac{1}{LC} q = 0 \text{ solve diff eq. ...}$$

$$\omega = \sqrt{\frac{1}{LC}} \text{ and } q = Q_0 \cos(\omega t + \phi) \text{ and } i = \frac{dq}{dt} = -\omega Q_0 \sin(\omega t + \phi)$$

$$\text{energy: } \frac{1}{2} L i^2 + \frac{q^2}{2C} = \frac{Q_0^2}{2C} \text{ solve for } i = \pm \sqrt{\frac{1}{LC}} \cdot \sqrt{Q_0^2 - q^2}$$

LRC circuit



LRC series circuit

Loses energy from R.

$$-iR - L \frac{di}{dt} - \frac{q}{C} = 0 \rightarrow \frac{d^2 q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q = 0 \quad q'' + \frac{R}{L} q' + \frac{1}{LC} q = 0$$


$$q = A e^{-(R/2L)t} \cos\left(\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}t + \phi\right)$$

corresponds to underdamped behavior. when this = 0
crit damp

$$\omega_{LRC}^2 = \frac{1}{LC} - \frac{R^2}{4L^2}$$

- less under
- more over

Rough Physics Notes

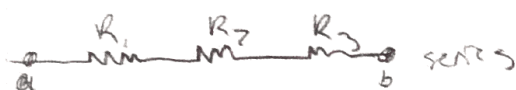

series



parallel

$R_{net} = R_{eq}$ * different notation

$$V_{ab} = \pm R_{net} I \text{ or } R_{net} = \frac{V_{ab}}{I}$$

Series $\rightarrow V_{ac} = V_{ax} + V_{xy} + V_{yb} = I(R_1 + R_2 + R_3) \rightarrow \frac{V_{ab}}{I} = R_1 + R_2 + R_3 \leftarrow R_{net}$

* SERIES Voltage not the same, current constant

Parallel \rightarrow

* Parallel current different, voltage constant


$$I_1 = \frac{V_{ab}}{R_1}, I_2 = \frac{V_{ab}}{R_2}, I_3 = \frac{V_{ab}}{R_3} \leftarrow \text{current splits up}$$

$$I_{net} = I_1 + I_2 + I_3 = V_{ab} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \text{ so } \frac{I_{net}}{V_{ab}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \rightarrow \frac{1}{R_{net}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Kirchoff Rules: * many circuits are just series-parallel combos

$\sum I = 0$ sum of currents through any junction

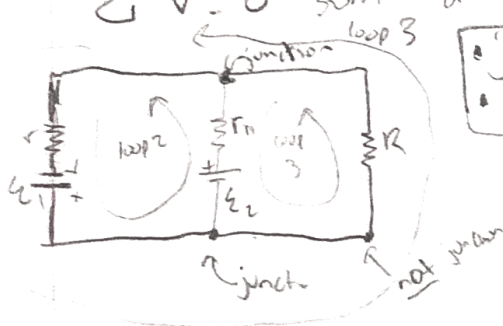$\sum V = 0$ sum of voltages through any loop



- junctions are where 3 or more conductors meet
- loop is any closed conducting path



a) sign conventions for emf
 $\xrightarrow{\text{travel}} = +\mathcal{E}$
 $\xleftarrow{\text{travel}} = -\mathcal{E}$

b) sign conventions for resistors
 $\xrightarrow{\text{travel}} = -IR$
 $\xleftarrow{\text{travel}} = +IR$

$\xrightarrow{\text{travel}} = -IR$
 $\xleftarrow{\text{travel}} = +IR$


* not necessary in the direction of the current!

goes in the direction of increasing potential

goes in the direction of decreasing potential

for battery loop example

$$\sum V = 0 \text{ in a loop}$$

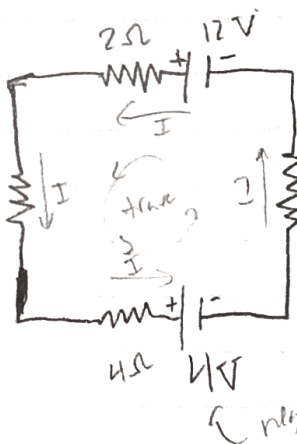

resistor or jumper cable and conduction path


through the car

current going from high potential to lower potential

* if you have multiple batteries guess which one will "overpower" then use Kirchhoff's rules

RL circuits

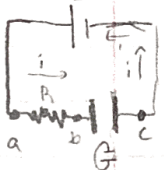- this is when all voltages, current, power change with time



this circuit charges a capacitor

- starts off uncharged until we turn it on.

- $V_{bc} \text{ (at } t=0) = 0$

- with Kirchhoff's loop rule $V_{ab} \text{ (at } t=0) = \varepsilon \Rightarrow I_0 = \frac{V_{ab}}{R} = \frac{\varepsilon}{R}$

↳ since V_{bc} is 0 then the voltage across a loop has to exist somewhere

- as capacitor charges, so V_{bc} increases, V_{ab} decreases ($V_{ab} + V_{bc} = \varepsilon$) \rightarrow corresponding to \downarrow current

- after a long time capacitor charges then $I \rightarrow 0$, then $V_{ab} \rightarrow 0$

- that means from $V_{ab} + V_{bc} = \varepsilon \rightarrow 0 + V_{bc} = \varepsilon \Rightarrow V_{bc} = \varepsilon$

Let q = charge on capacitor, i be the current in the circuit,


and the instantaneous potential differences V_{ab} and V_{bc} are: $V_{ab} = iR$, $V_{bc} = \frac{q}{C}$

Kirchhoff loop rule: $\varepsilon - iR - \frac{q}{C} = 0 \Rightarrow i = \frac{\varepsilon}{R} - \frac{q}{RC}$

at $t=0 \rightarrow q=0 \rightarrow i=0$ substituting in $i=0$ for $I_0 = \frac{\varepsilon}{R}$ (as we have already noted, good check)

as q increases $\frac{q}{RC}$ increases, and q approaches full charge, let's call it Q_f , then $i=0$

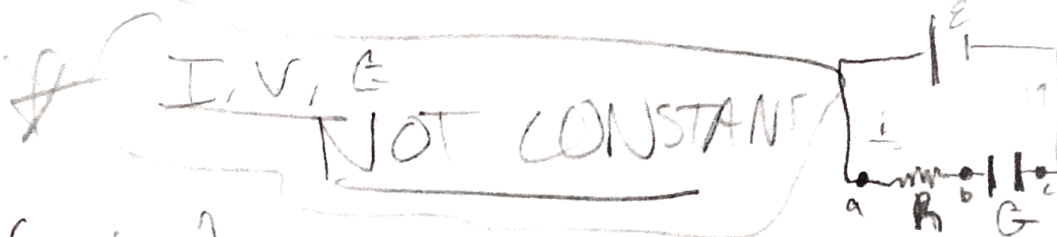so you get $\frac{\varepsilon}{R} = \frac{Q_f}{RC}$ when q is fully charged, simplify, $Q_f = C\varepsilon$



RC circuits continued

General function of charge q and current i as functions of time

Using equation $i = \frac{\epsilon}{R} - \frac{q}{RC}$ (from Kirchhoff rule $\sum V = 0$ through loop $-\epsilon - iR - \frac{q}{C} = 0$)
 $\frac{dq}{dt} = \frac{\epsilon}{R} - \frac{q}{RC} = -\frac{1}{RC} (q - C\epsilon)$
 $\frac{\epsilon}{R} = \frac{q_0}{RC} \Rightarrow q_0 = C\epsilon$

Rearrange to: $\frac{1}{q - C\epsilon} dq = -\frac{1}{RC} dt$

Integrate: $\int_0^q \frac{dq}{q - C\epsilon} = -\int_0^t \frac{dt}{RC} \Rightarrow \ln\left(\frac{q - C\epsilon}{-C\epsilon}\right) = -\frac{t}{RC}$

then $\frac{-t/RC}{e} = \frac{q - C\epsilon}{0 - C\epsilon} \Rightarrow q = C\epsilon(1 - e^{-t/RC}) = Q_0(1 - e^{-t/RC})$
 $Q_0 = C\epsilon$

and $i = \frac{dq}{dt} = \frac{\epsilon}{R} e^{-t/RC} = I_0 e^{-t/RC}$
capacitor time since it was turned on
at $t=0$ $q=0$ $i = \frac{\epsilon}{R}$

when $t = RC$ in i has decayed to $\frac{1}{e}$, and $q = (1 - \frac{1}{e})$ of its final value $Q_0 = C\epsilon$
 RC is the a measure of how quickly the capacitor charges
 $RC =$ the constant or relaxation time

$\tau = RC$, where τ is small capacitor charges quick, τ is larger, charging is slow

discharging a capacitor

now lets say a C has an initial charge Q_0 then we remove the emf, so

now use $i = \frac{dq}{dt} = \frac{\epsilon}{R} - \frac{q}{RC}$ but $\epsilon = 0$ so $i = \frac{dq}{dt} = -\frac{q}{RC}$
 $I_0 = -\frac{Q_0}{RC}$
 $\int_{Q_0}^q \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt \Rightarrow \ln\left(\frac{q}{Q_0}\right) = -\frac{t}{RC} \Rightarrow q = Q_0 e^{-t/RC}$

$i = \frac{dq}{dt} = -\frac{Q_0}{RC} e^{-t/RC} = I_0 e^{-t/RC}$


$P = \epsilon i = i^2 R$, resistor $V_{RC} =$ (voltage across $C = \frac{q}{C} \rightarrow$ multiply by $i \rightarrow \frac{iq}{C} = V_{RC} i$

using $\epsilon = iR + \frac{q}{C}$, multiply by $i \rightarrow i\epsilon = i^2 R + \frac{i q}{C}$

From $\frac{1}{2} QV \rightarrow Q_0 \frac{\epsilon}{2}$ so $\frac{1}{2}$ of ϵ stored in capacitor, the other half dissipated by R
 $P_{\text{tot}} = P_{\text{diss by } R} + P_{\text{capacitor}}$
Power stored by C


* if you travel in direction of current through resistor you lose V
vice versa

loop rule in circuits


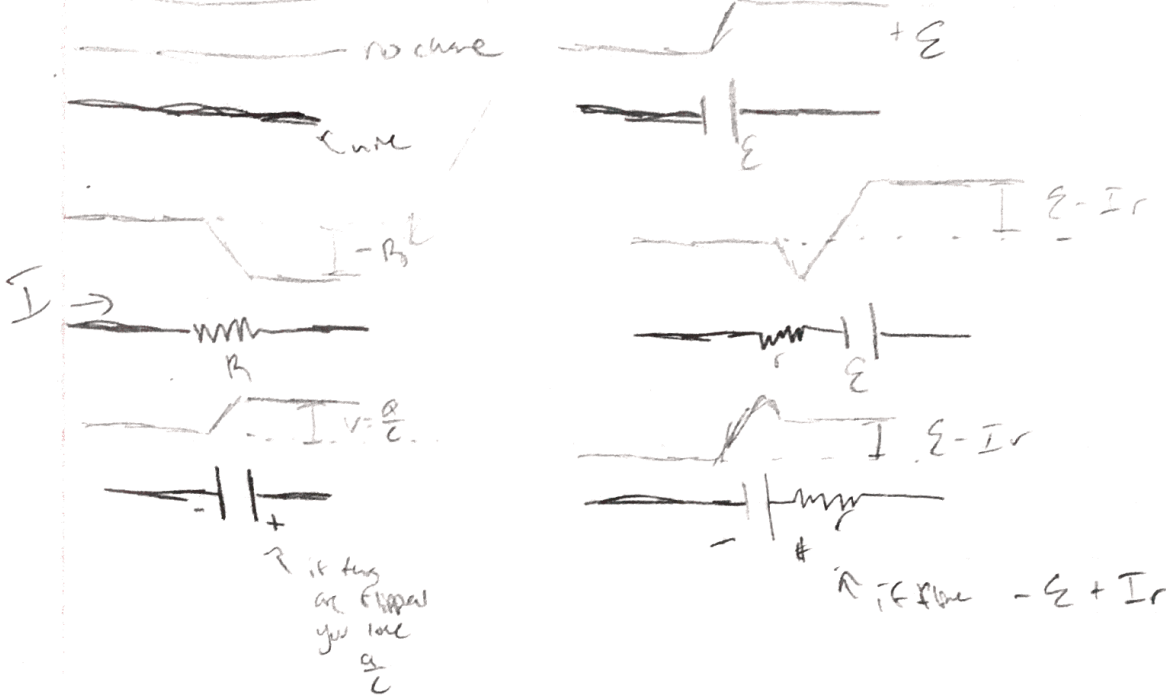


Charger Battery P1.2

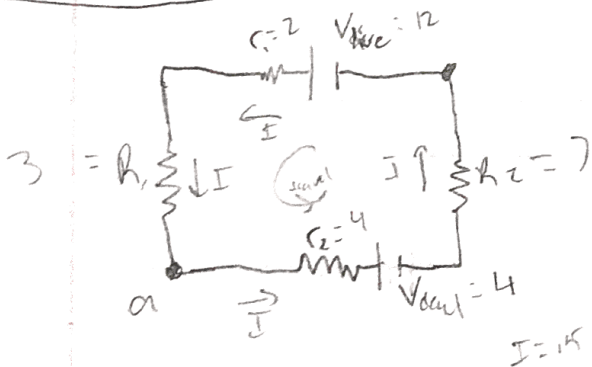red w/ dead to the pos to pos
then from live neg to dead neg (usually bad)
so don't connect directly
but through a metal piece


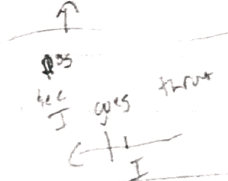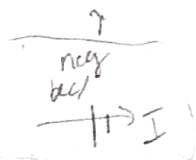
$$\sum V = 0 = -4 - 4I - 7I + 12 - 2I - 3I = 0$$



$$I = 1.5A$$

$$P_{in} = V \cdot I = (V_{live} - I r) I = (12 - 2I) I = 5.5W$$

$$P_{dead} = V \cdot I = (V_{dead} - I r) I = (-4 - 4I) I = -3W$$


$$P_{R1} = V \cdot I = -3I I = -3I^2 = -7.5W$$

$$P_{R2} = V \cdot I = -7I I = -4.75W$$

$$V_a - 4 - 4I - 7I = V_b$$

$$V_a - 4 - 11I = V_b$$

$$V_a - V_b = 4 + 11I = 9.6V$$

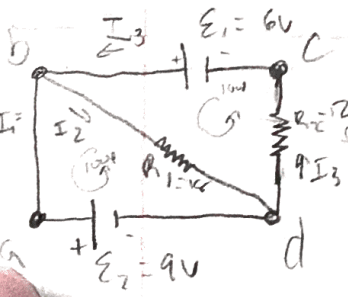

$$\sum I_{in} = \sum I_{out} \Rightarrow I_3 = I_1 + I_2$$

$$0 = -12I_2 + 9 \Rightarrow I_2 = 0.75A$$

$$0 = -I_2 \cdot 12 - 12I_3 + 6 \Rightarrow I_3 = -0.25A$$

$$I_1 = +0.25A$$

